

600V LARGE DIIPM Ver.6 Series APPLICATION NOTE

PSS**SA2F6

Table of contents

CHAPTER 1 INTRODUCTION	2
1.1 Target Applications	2
1.2 Product Line-up	2
1.3 Functions and Features	2
1.4 The Differences of Previous Series (600V Large DIIPM Ver.4) and This Series	3
CHAPTER 2 SPECIFICATIONS AND CHARACTERISTICS	4
2.1 Specifications	4
2.1.1 Maximum Ratings	4
2.1.2 Thermal Resistance	5
2.1.3 Electric Characteristics (Power Part)	6
2.1.4 Electric Characteristics (Control Part)	7
2.1.5 Recommended Operating Conditions	8
2.1.6 Mechanical Characteristics and Ratings	9
2.2 Protective Functions and Operating Sequence	10
2.2.1 Short Circuit Protection	10
2.2.2 Control Supply UV Protection	14
2.2.3 Temperature Output Function	16
2.3 Package Outlines	21
2.3.1 Outline Drawing	21
2.3.2 Power Chip Position	22
2.3.3 Marking Position	22
2.3.4 Terminal Description	23
2.4 Mounting Method	25
2.4.1 Electric Spacing	25
2.4.2 Mounting Method and Precautions	25
2.4.3 Soldering Conditions	26
CHAPTER 3 SYSTEM APPLICATION HIGHLIGHT	27
3.1 Application Guidance	27
3.1.1 System Connection	27
3.1.2 Interface Circuit (Direct Coupling Interface example)	28
3.1.3 Interface Circuit (Opto-coupler Isolated Interface)	29
3.1.4 Circuits of Signal Input terminals and Fo Terminal	30
3.1.5 Snubber Circuit	32
3.1.6 Influence of Wiring	33
3.1.7 Precaution for Wiring on PCB	34
3.1.8 SOA of DIIPM	35
3.1.9 SCSOA	36
3.1.10 Power Life Cycles	37
3.2 Power Loss and Thermal Dissipation Calculation	38
3.2.1 Power Loss Simulation	38
3.2.2 Temperature Rise Considerations and Calculation Example	40
3.3 Noise and ESD Withstand Capability	41
3.3.1 Evaluation Circuit of Noise Withstand Capability	41
3.3.2 Countermeasures and Precautions	41
3.3.3 Static Electricity Withstand Capability	42
CHAPTER 4 Bootstrap Circuit Operation	43
4.1 Bootstrap Circuit Operation	43
4.2 Bootstrap Supply Circuit Current at Switching State	44
4.3 Note for designing the bootstrap circuit	45
4.4 Initial charging in bootstrap circuit	46
CHAPTER 5 PACKAGE HANDLING	47
5.1 Packaging Specification	47
5.2 Handling Precautions	48

CHAPTER 1 INTRODUCTION

1.1 Target Applications

Motor drives for industrial use, such as packaged air conditioners, general-purpose inverter, servo, except for automotive applications.

1.2 Product Line-up

Table 1-1 Line-up

Type Name	IGBT Rating	Motor Rating (Note 1)	Isolation Voltage
PSS50SA2F6	50A/600V	3.7kW / 220V _{AC}	V _{iso} = 2500Vrms (Sine 60Hz, 1min All shorted pins-heat sink)
PSS75SA2F6	75A/600V	5.5kW / 220V _{AC}	

Note 1: These motor ratings are general ratings, so those may be changed by conditions.

1.3 Functions and Features

600V Large DIIPM Ver.6 is a compact intelligent power module with transfer molding package favorable for larger mass production. And it includes power chips, drive and protection circuits.

This series apply same package, which has high thermal radiation performance by the insulated sheet structure, and pin compatibility with current Large DIIPM Ver.4 series. In addition, this series newly integrate low loss 7th generation IGBT optimized for DIIPM and 600V bootstrap diodes for generating P-side driver 15V supply.

Large DIIPM Ver.6 will contribute to improve system efficiency, cost and also design time.

Outline photograph and internal cross-section structure are described in Fig.1-1 and Fig.1-2.

 


Fig.1-1 Package outline

 


Fig.1-2 Internal cross-section structure

Features:

- For P-side IGBTs
 - Drive circuit
 - High voltage level shift circuit
 - Control supply under voltage (UV) protection circuit (without fault signal output)
 - Built-in bootstrap diode with current limiting resistor
- For N-side IGBTs
 - Drive circuit
 - Short circuit (SC) protection circuit (by detecting sense current divided at N-side IGBT with external sense resistor)
 - Control supply under voltage (UV) protection circuit (with fault signal output)
 - Analog output of LVIC temperature
- Fault Signal Output
 - Corresponding to SC protection and N-side UV protection
- IGBT Drive Supply
 - Single DC15V power supply
- Control Input Interface
 - Schmitt-triggered 3V, 5V input compatible, High active logic
- UL Recognized
 - UL1557 File E323585

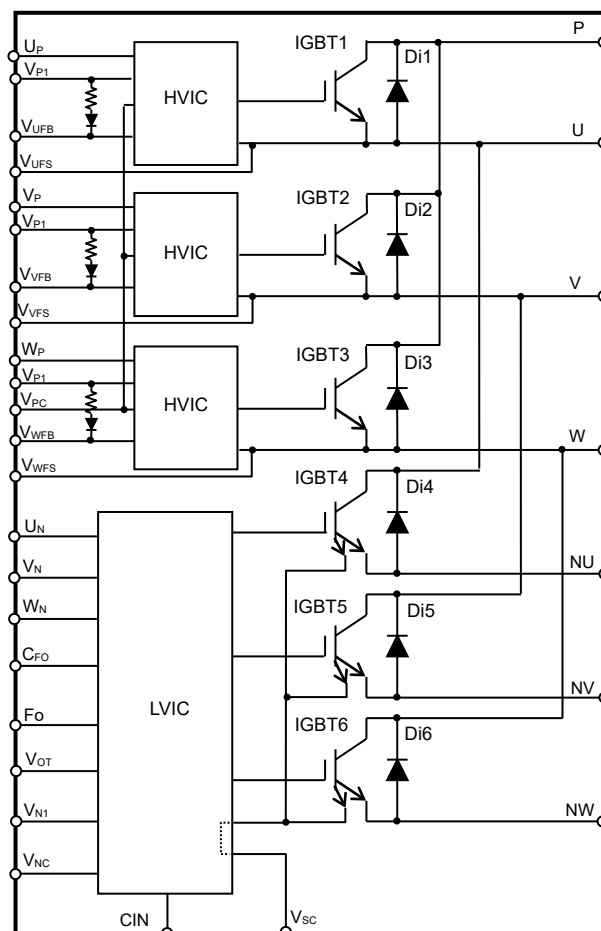


Fig.1-3 Internal circuit schematic

1.4 The Differences of Previous Series (600V Large DIIPM Ver.4) and This Series

There are some differences between this Ver.6 series and former Ver.4 series (PS21A7*) as below Table 1-2.

Table 1-2 Differences of specifications

Item	Ver.4		Ver.6		Ref.
	PS21A79	PS21A7A	PSS50SA2F6	PSS75SA2F6	
	50A	75A	50A	75A	
Built-in IGBT	5 th generation IGBT (LPT-CSTBT)		7 th generation IGBT (LPT-CSTBT)		-
Bootstrap Di	Nothing		Built-in (with current limit R typ. 20Ω)		-
Temperature output (V _{OT} Output)	typ. 3.63V (at LVIC temp. = 85°C)		typ. 2.38V (at LVIC temp. = 75°C) with pull down resistor		Section 2.2.3
Fault output current I _{FO}	max. 1mA		max. 5mA (Direct coupler drive is available)		Section 3.1.4
Arm shoot through blocking time	Min. 2.2μs	Min. 2.7μs	Min. 2.2μs	Min. 2.4μs	
T _j	-20°C ~150°C		-30°C ~150°C		
T _c	-20°C ~100°C		-30°C ~125°C		

There are other differences. (e.g. electric characteristics, sense resistance for SC protection, allowable minimum pulse width and electrical potential of dummy terminals) Please refer each datasheet for more detail.

CHAPTER 2 SPECIFICATIONS AND CHARACTERISTICS

2.1 Specifications

The specifications are described below by using PSS75SA2F6 (75A/600V) as an example. Please refer to respective datasheet for the detailed description of other types.

2.1.1 Maximum Ratings

The maximum ratings of PSS75SA2F6 are shown in Table 2-1.

Table 2-1 Maximum Ratings of PSS75SA2F6

MAXIMUM RATINGS ($T_j = 25^\circ\text{C}$, unless otherwise noted)

INVERTER PART

Symbol	Parameter	Condition	Ratings	Unit	
V_{CC}	Supply voltage	Applied between P-NU,NV,NW	450	V	← (1)
$V_{CC(surge)}$	Supply voltage (surge)	Applied between P-NU,NV,NW	500	V	← (2)
V_{CES}	Collector-emitter voltage		600	V	← (3)
$\pm I_C$	Each IGBT collector current	$T_C = 25^\circ\text{C}$ (Note 1)	75	A	← (4)
$\pm I_{CP}$	Each IGBT collector current (peak)	$T_C = 25^\circ\text{C}$, up to 1ms	150	A	
T_j	Junction temperature		-30~+150	$^\circ\text{C}$	← (5)

Note 1: Pulse width and period are limited due to junction temperature.


CONTROL (PROTECTION) PART

Symbol	Parameter	Condition	Ratings	Unit
V_D	Control supply voltage	Applied between $V_{P1}-V_{PC}$, $V_{N1}-V_{NC}$	20	V
V_{DB}	Control supply voltage	Applied between $V_{UFB}-V_{UFS}$, $V_{VFB}-V_{VFS}$, $V_{WFB}-V_{WFS}$	20	V
V_{IN}	Input voltage	Applied between U_P , V_P , W_P-V_{PC} , U_N , V_N , W_N-V_{NC}	-0.5~ $V_D+0.5$	V
V_{FO}	Fault output supply voltage	Applied between F_O-V_{NC}	-0.5~ $V_D+0.5$	V
I_{FO}	Fault output current	Sink current at F_O terminal	5	mA
V_{SC}	Current sensing input voltage	Applied between $CIN-V_{NC}$	-0.5~ $V_D+0.5$	V

TOTAL SYSTEM

Symbol	Parameter	Condition	Ratings	Unit	
$V_{CC(prot)}$	Self protection supply voltage limit (Short circuit protection capability)	$V_D = 13.5\sim 16.5\text{V}$, Inverter Part $T_i = 150^\circ\text{C}$, non-repetitive, up to 2 μs	400	V	← (6)
T_C	Module case operation temperature	(Note 2)	-30~+125	$^\circ\text{C}$	
T_{stg}	Storage temperature		-40~+125	$^\circ\text{C}$	
V_{iso}	Isolation voltage	60Hz, Sinusoidal, AC 1min, between connected all pins and heat sink plate	2500	V_{rms}	

Note 2: T_C measurement point

 

[Item explanation]

- (1) V_{CC} The maximum P-N voltage in no switching state. Voltage suppressing circuit such as a brake circuit is necessary if the voltage exceeds this value.
- (2) $V_{CC(surge)}$ The maximum P-N surge voltage in switching state. Snubber circuit is necessary if the voltage exceeds $V_{CC(surge)}$.
- (3) V_{CES} The maximum sustained collector-emitter voltage of built-in IGBT.
- (4) $\pm I_C$ The allowable current flowing into collect electrode (@ $T_C=25^\circ\text{C}$).Pulse width and period are limited due to junction temperature T_j .
- (5) T_j The maximum junction temperature rating is 150°C . Please design its junction temperature so that it doesn't exceed 150°C including the ripple during continuous operation. Repetitive temperature variation ΔT_j affects the life time of power cycle, so refer life time curves (Section 3.1.10) for safety design.
- (6) $V_{CC(prot)}$ The maximum supply voltage for IGBT turning off safely in case of an SC fault. The power chip might be damaged if supply voltage exceeds this rating.
- (7) T_C position T_C (case temperature) is defined as the temperature just underneath the specified power chip. Please mount a thermocouple on the heat sink surface at above position to get proper temperature. Due to the control schemes (e.g. Different control between P and N-side like two phase modulation, high-side chopping), the highest T_C point may be different from above point. In such cases, it is necessary to change the measuring point to that under the highest power chip. (Refer Section 2.3.2)

2.1.2 Thermal Resistance

Table 2-2 shows the thermal resistance.

Table 2-2 Thermal resistance of PSS75SA2F6

THERMAL RESISTANCE

Symbol	Parameter	Condition	Limits			Unit
			Min.	Typ.	Max.	
$R_{th(j-c)Q}$	Junction to case thermal resistance (Note 1)	Inverter IGBT part (per 1/6 module)	-	-	0.77	K/W
$R_{th(j-c)F}$		Inverter FWDi part (per 1/6 module)	-	-	1.25	K/W

Note 1: Grease with good thermal conductivity and long-term endurance should be applied evenly with about +100 μ m~+200 μ m on the contacting surface of DIIPM and heat sink. The contacting thermal resistance between DIIPM case and heat sink $R_{th(c-f)}$ is determined by the thickness and the thermal conductivity of the applied grease. For reference, $R_{th(c-f)}$ is about 0.2K/W (per 1/6 module, grease thickness: 20 μ m, thermal conductivity: 1.0W/m·k).

The above data shows the thermal resistance between chip junction and case at steady state. The thermal resistance goes into saturation in about 10s. The thermal resistance under 10s is called as transient thermal impedance which is shown in Fig.2-1. $Z_{th(j-c)}^*$ is the normalized value of the transient thermal impedance. ($Z_{th(j-c)}^* = Z_{th(j-c)} / R_{th(j-c)max}$) For example, the IGBT transient thermal impedance of PSS75SA2F6 in 0.1s is $0.77 \times 0.5 = 0.39$ K/W.

The transient thermal impedance isn't used for constantly current, but for short period current (ms order). (E.g. In the cases at motor starting, at motor lock...)

 


Fig.2-1 Typical transient thermal impedance

2.1.3 Electric Characteristics (Power Part)

Table 2-3 shows the typical static characteristics and switching characteristics.

Table 2-3 Static characteristics and switching characteristics of PSS75SA2F6

Inverter Part

Symbol	Parameter	Condition		Limits			Unit
				Min.	Typ.	Max.	
$V_{CE(sat)}$	Collector-emitter saturation voltage	$V_D=V_{DB} = 15V, V_{IN}= 5V, I_C= 75A$	$T_J= 25^{\circ}C$	-	1.30	1.60	V
			$T_J= 125^{\circ}C$	-	1.40	1.70	
V_{EC}	FWDi forward voltage	$V_{IN}= 0V, -I_C= 75A$		-	1.70	2.20	V
t_{on}	Switching times	$V_{CC}= 300V, V_D= V_{DB}= 15V$ $I_C= 75A, T_J= 125^{\circ}C, V_{IN}= 0\leftrightarrow 5V$ Inductive Load (upper-lower arm)		1.20	1.80	2.40	μs
$t_{C(on)}$				-	0.40	0.65	μs
t_{off}				-	2.80	3.60	μs
$t_{C(off)}$				-	0.30	0.60	μs
t_{rr}				-	0.30	-	μs
I_{CES}	Collector-emitter cut-off current	$V_{CE}=V_{CES}$	$T_J= 25^{\circ}C$	-	-	1	mA
			$T_J= 125^{\circ}C$	-	-	10	

Switching time definition and performance test method are shown in Fig.2-2 and 2-3.



 
 


Fig.2-2 Switching time definition

 

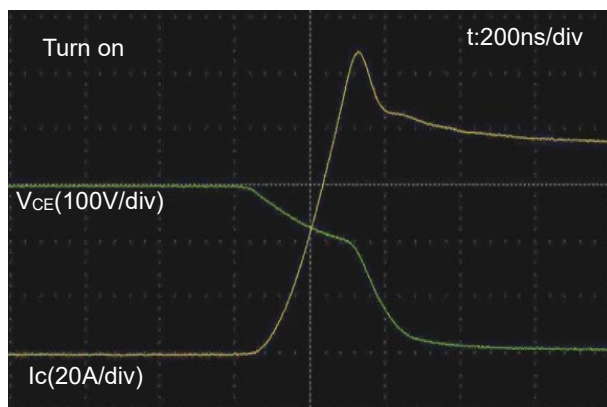Short A for N-side IGBT, and short B for P-side IGBT evaluation
Fig.2-3 Evaluation circuit (inductive load)



Conditions: $V_{CC}=300V$, $V_D=V_{DB}=15V$, $T_J=125^{\circ}C$, $I_C=75A$, Inductive load half-bridge circuit

Fig.2-4 Typical switching waveform

2.1.4 Electric Characteristics (Control Part)

Table 2-4 Control (Protection) characteristics of PSS75SA2F6

CONTROL (PROTECTION) PART

Symbol	Parameter	Condition		Limits			Unit
				Min.	Typ.	Max.	
I _D	Circuit current	Total of V _{P1} -V _{PC} , V _{N1} -V _{NC}	V _D =15V, V _{IN} =0V	-	-	5.50	mA
			V _D =15V, V _{IN} =5V	-	-	5.50	
I _{DB}		Each part of V _{UFB} -V _{UFS} , V _{VFB} -V _{VFS} , V _{WFB} -V _{WFS}	V _D =V _{DB} =15V, V _{IN} =0V	-	-	0.55	
			V _D =V _{DB} =15V, V _{IN} =5V	-	-	0.55	
I _{SC}	Short circuit trip level	Rs= 20.0Ω (±1%), Without outer shunt resistors to NU,NV,NW (Note 1) terminals		127	-	-	A
UV _{DBt}	P-side Control supply under-voltage protection(UV)		Trip level	10.0	-	12.0	V
UV _{DBr}			Reset level	10.5	-	12.5	V
UV _{Dt}	N-side Control supply under-voltage protection(UV)		Trip level	10.3	-	12.5	V
UV _{Dr}			Reset level	10.8	-	13.0	V
V _{FOH}	Fault output voltage	V _{SC} = 0V, F _O terminal pulled up to 5V by 10kΩ		4.9	-	-	V
V _{FOL}		V _{SC} = 1V, I _{FO} = 1mA		-	-	0.95	V
t _{FO}	Fault output pulse width	C _{FO} =22nF (Note 2)		1.6	2.4	-	ms
I _{IN}	Input current	V _{IN} = 5V		0.7	1.0	1.5	mA
V _{th(on)}	ON threshold voltage	Applied between U _P , V _P , W _P , U _N , V _N , W _N -V _{NC}		-	2.1	2.6	V
V _{th(off)}	OFF threshold voltage			0.8	-	-	
V _{OT}	Temperature output	LVIC temperature=75°C,Pull down R=5.1kΩ (Note 3)		2.26	2.38	2.51	V
V _F	Bootstrap Di forward voltage	I _F =10mA including voltage drop by limiting resistor		0.5	0.9	1.3	V
R	Built-in limiting resistance	Included in bootstrap Di		16	20	24	Ω

Note 1: Short circuit protection detects sense current divided from main current at N-side IGBT and works for N-side IGBT only. In the case that outer shunt resistor is inserted into main current path, protection current level I_{SC} changes. For details, please refer the section about SC protection in this document.

2: Fault signal is output when short circuit or N-side control supply under-voltage protection works. The fault output pulse-width t_{FO} depends on the capacitance of C_{FO} . ($C_{FO} (typ.) = t_{FO} \times (9.1 \times 10^{-6}) [F]$)

3: DIIPM doesn't shut down IGBTs and output fault signal automatically when temperature rises excessively. When temperature exceeds the protective level that user defined, controller (MCU) should stop the DIIPM immediately.

***) Some specifications differs according to its rated current. For more details, please refer to the datasheet for each product.**

2.1.5 Recommended Operating Conditions

The recommended operating conditions are described in Table 2-5. Although these conditions are the recommended but not the necessary ones, it is highly recommended to operate the modules within these conditions so as to ensure DIIPM safe operation.

Table 2-5 Recommended operating conditions of PSS75SA2F6

RECOMMENDED OPERATION CONDITIONS


Symbol	Parameter	Condition	Limits			Unit
			Min.	Typ.	Max.	
V_{CC}	Supply voltage	Applied between P-NU, NV, NW	0	300	400	V
V_D	Control supply voltage	Applied between $V_{P1}-V_{PC}$, $V_{N1}-V_{NC}$	13.5	15.0	16.5	V
V_{DB}	Control supply voltage	Applied between $V_{UFB}-V_{UFS}$, $V_{VFB}-V_{VFS}$, $V_{WFB}-V_{WFS}$	13.0	15.0	18.5	V
ΔV_D , ΔV_{DB}	Control supply variation		-1	-	+1	V/ μ s
t_{dead}	Arm shoot-through blocking time	For each input signal	2.4	-	-	μ s
f_{PWM}	PWM input frequency	$T_C \leq 100^\circ\text{C}$, $T_J \leq 125^\circ\text{C}$	-	-	20	kHz
PWIN(on)	Minimum input pulse width	(Note 4) (Note 5)	1.5	-	-	μ s
PWIN(off)			3.0	-	-	
V_{NC}	V_{NC} variation	Between $V_{NC}-NU$, NV, NW (including surge)	-5.0	-	+5.0	V

Note 4 : DIIPM might not make response if the input signal pulse width is less than PWIN(on).

 5: DIIPM might make no response or delayed response (P-side IGBT only) for input pulse width less than PWIN(off).

Over rated collector current (I_C) operation, DIIPM might make delayed response even if the input signal pulse width is more than PWIN(off).

About Delayed Response Against Shorter Input Off Signal Than PWIN(off) (P-side only)



***) Some specifications differs according to its rated current. For more details, please refer to the datasheet for each product.**

2.1.6 Mechanical Characteristics and Ratings

The mechanical characteristics and ratings are shown in Table 2-6.
Please refer to Section 2.4 for the detailed mounting instruction.


Table 2-6 Mechanical characteristics and ratings of PSS75SA2F6

MECHANICAL CHARACTERISTICS AND RATINGS

Parameter	Condition	Reference	Limits			Unit
			Min.	Typ.	Max.	
Mounting torque	Mounting screw : M4 (Note 6)	JEITA-ED-4701 402 method II	0.98	1.18	1.47	N·m
Terminal strength pulling	Load 20N	JEITA-ED-4701 401 method I	10	-	-	s
Terminal strength bending	Load 10N, 90deg. bend	JEITA-ED-4701 401 method III	2	-	-	times
Weight			-	46	-	g
Heat radiation part flatness			-50	-	100	μm

Note 6: Plain washers (ISO 7089~7094) are recommended.

Measurement point of heat-sink flatness

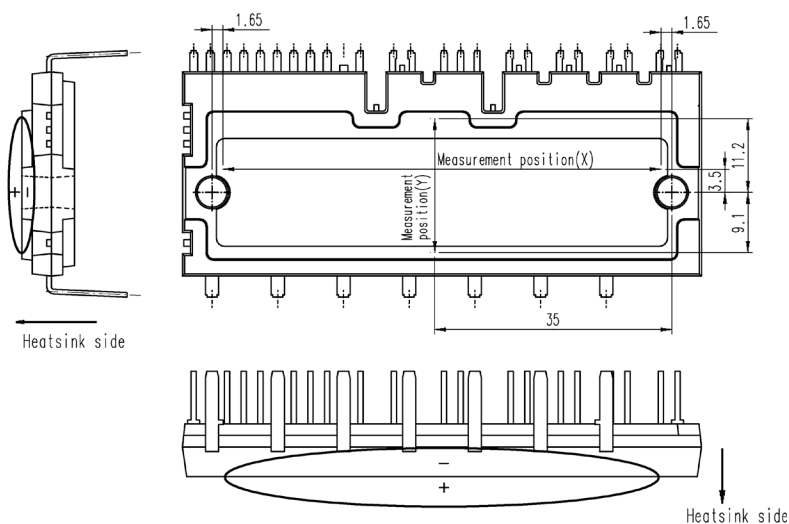


2.2 Protective Functions and Operating Sequence

There are SC protection, UV protection and outputting LVIC temperature function in this series.
The detailed information is described below.

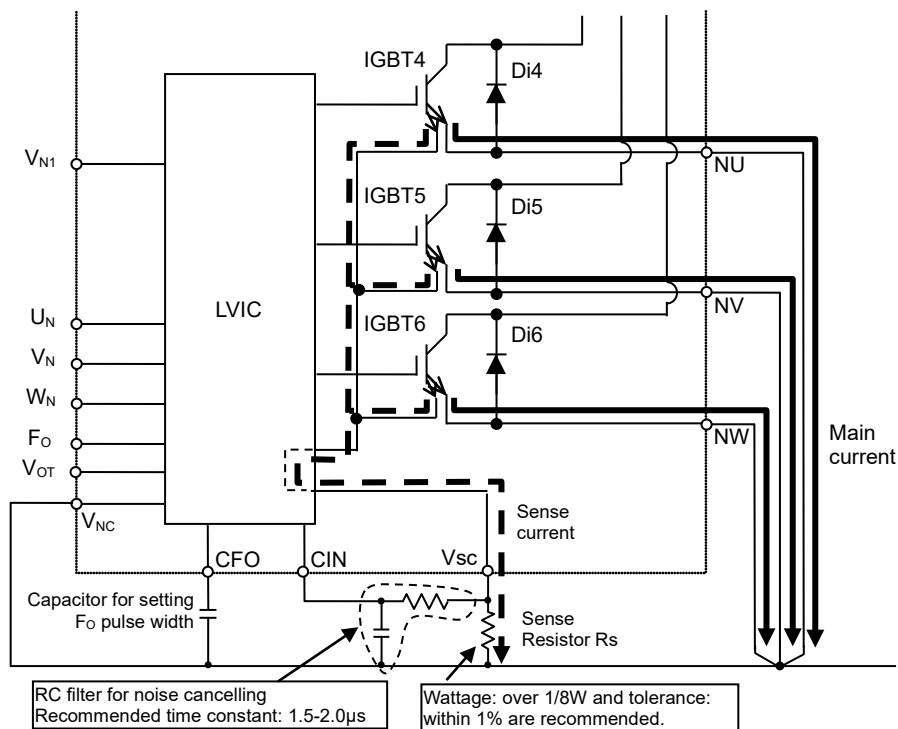2.2.1 Short Circuit Protection

This series apply the detection method of small sense current, which is divided at N-side IGBT, to SC protection.
So high wattage type shunt resistor isn't necessary for SC protection. (Fig.2-5)



*) This wattage of sense resistor is described as a guide, so it is recommended to evaluate on your real system well.

Fig.2-5 SC protection circuit

SC protection works by inputting the potential, which is generated by sense current flowing into the sense resistor, to the CIN terminal. Tabel 2-7 describes specified sense resistance and minimum SC protection current in that case for each products.

When SC ptotection works, DIIPM shuts down all N-side IGBTs hardly and outputs Fo signal. Its pulse width(t_{Fo}) is set by C_{Fo} capacitor ($C_{Fo} = t_{Fo} \times 9.1 \times 10^{-6} [F]$).

To prvent malfunction, it is recommended to insert RC filter before inputting to CIN terminal and set the time constant to shut down withiin $2\mu s$ when short circuit occurs. (Time constant $1.5\mu s$ - $2.0\mu s$ is recommended.) Also it is necessary to set the resistance of RC filter to ten or more times of the sense resistor R_s . (Hundred times is recommended.)

Table 2-7 SC protection trip level (Not connecting outer shunt resistors to NU,NV,NW terminals.)

Type name	R_s	Min.
PSS75SA2F6	20.0Ω	127A
PSS50SA2F6	31.6Ω	85A

For sense resistor, its large fluctuation leads to large fluctuation of SC trip level. So it is necessary to select small variation and good temperature characteristic type (within $\pm 1\%$ is recommended).

Wattage of the sense resistor can be estimated in view of the fact that the maximum split ratio between the main and sense currents is about 4000:1. (In this case maximum sense current flows.)

The estimation example for PSS75SA2F6 is described as below.

[Estimation example]

(1) Normal operation state

It is assumed that the maximum main current for normal operation is 75A (rated current, for keeping a margin) and the sense resistance is 20.0Ω.

In this case, The maximum sense current flows through the sense resistor is calculated as below.

$$75\text{A} / 4000 = 18.8\text{mA}$$

And the loss at the sense resistor is

$$P = I^2 \cdot R \cdot t = (18.8\text{mA})^2 \times 20.0\Omega = \underline{7.0\text{mW}}$$

(2) Short circuit state

When short circuit occurs, its current depends on the condition, but up to IGBT saturation current (about 10 times of the rated current =350A) flows. So the sense current is

$$750\text{A} / 4000 = 187.5\text{mA}$$

But this current shut down within 2μs by SC protection. And the average loss at the sense resistor is

$$P = I^2 \cdot R \cdot t = (187.5\text{mA})^2 \times 20.0\Omega \times 2\mu\text{s} / 1\text{s} = \underline{0.0014\text{mW}}$$

And drop voltage of this sense resistor is

$$V = 187.5\text{mA} \times 20.0\Omega = 3.8\text{V}$$

As explained above, over 0.03W wattage resistor will be suitable, but it is necessary to confirm on your real system finally.

[Remarks]

It takes more time (Table 2-8) from inputting over threshold voltage to CIN terminal to shutting down IGBTs. (Because of IC's transfer delay)

Table 2-8 Internal time delay of IC

Item	typ	max	Unit
IC transfer delay time	0.5	1.0	μs

Therefore, the total delay time from short circuit occurring to shutting down IGBTs is the sum of the delay by the outer RC filter and this IC delay.

[SC protection (N-side only)]

a1. Normal operation: IGBT ON and outputs current.

a2. Short circuit current detection (SC trigger) (It is recommended to set RC time constant 1.5~2.0μs so that IGBT shut down within 2.0μs when SC.)

a3. All N-side IGBTs' gates are hard interrupted.

a4. All N-side IGBTs turn OFF.

a5. Fo outputs with a fixed pulse width determined by the external capacitance C_{FO}.

a6. Input "L": IGBT off.

a7. Fo finishes output, but IGBTs don't turn on until inputting next ON signal (L→H).

(IGBT of each phase can return to normal state by inputting ON signal to each phase.)

a8. Normal operation: IGBT ON and outputs current.

 


Fig.2-6 SC protection timing chart

[About Short Circuit Protection by Sense IGBT]

This function aims to protect from Short Circuit like arm short or load short. If high accuracy of protection current level (e.g. protection for demagnetizing motor) is necessary, it is recommended to apply the method by detecting the voltage at outer shunt resistors into main current path. In that case, the current split ratio between main and sense currents varies, thus minimum SC protection trip level changes from the value in Table 2-7. Therefore, adjustment of the sense resistance will be needed. The example of minimum SC trip level with outer shunt resistor is described in Table 2-9 (PSS75SA2F6, at sense resistance 20.0Ω). Please contact us about selecting sense resistance in the case of inserting outer shunt resistors.

Table 2-9 SC protection trip level (PSS75SA2F6, sense resistance 20.0Ω)

Outer shunt resistance	Minimum SC trip level
Nothing	127A
3mΩ	100A

It is recommended to set outer shunt resistance to the value as shown in Table 2-10 or less because too large shunt resistance causes decrease of IGBT saturation current by decreasing gate voltage at large current. (Large current makes large voltage drop at shunt resistor.) For shunt resistor, select low parasitic inductance resistor like surface mounted device type and pattern the wiring from the N-side emitter (NU, NV, NW) terminals as short as possible because of reducing surge by shutdown at large short circuit current.

Table 2-10 Recommended maximum outer shunt resistance

Type name	Rs
PSS75SA2F6	5mΩ
PSS50SA2F6	7mΩ

As a method that combines short circuit and over current protection function, there is a method which doesn't use sense resistor too. It is the same method as former DIIPM Ver.3 and the example of protection circuit is described in Fig.2-7.

The SC protection trip level is needed to set to double the rated current or less. And it is recommended to set the reference voltage of comparators to about 0.5V and select the shunt resistance in order that the SC trip level becomes double the rated current or less. (e.g. In the case that the protection level is set to double the rated current for PSS75SA2F6, $R=0.5V/150A=3.3m\Omega$ or more)

When this protection method is applied, the rated sense resistor Rs should be connected between Vsc terminal and GND for protecting from surge too. (Don't leave it open.)

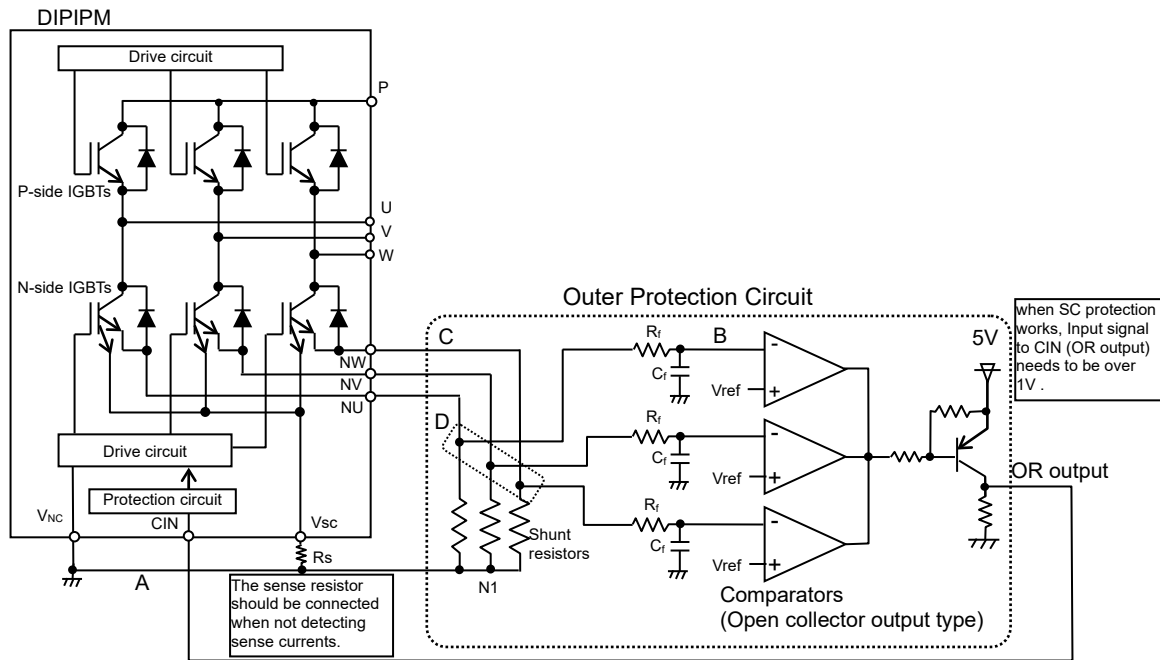


Fig.2-7 Example of SC protection circuit without detecting sense current.

Note:

- It is necessary to set the time constant $R_t C_t$ of external comparator input so that IGBT can stop within $2\mu s$ when short circuit occurs. SC interrupting time might vary with the wiring pattern, comparator speed and so on. If additional RC filter is inserted into OR output, it is necessary to consider its delay too.
- The threshold voltage V_{ref} is recommended to set about 0.5V.
- Select the shunt resistance so that SC trip-level is less than double the rated current.
- To avoid malfunction, the wiring A, B, C should be as short as possible.
- The point D at which the wiring to comparator is divided should be near the terminal of shunt resistor.
- OR output high level should be over 1V at all temperature range.

2.2.2 Control Supply UV Protection

The UV protection is designed for preventing unexpected operating behavior as described in Table 2-11.

Both P-side and N-side have UV protecting function. However, fault signal (Fo) output only corresponds to N-side UV protection. Fo output continuously during UV state.

In addition, there is a noise filter (typ. 10 μ s) integrated in the UV protection circuit to prevent instantaneous UV erroneous trip. Therefore, the control signals are still transferred in the initial 10 μ s after UV happened.

Table 2-11 DIIPM operating behavior versus control supply voltage

Control supply voltage	Operating behavior
0-4V (P, N)	Equivalent to zero power supply. UV function is inactive, no Fo output. Normally IGBT does not work. But, external noise may cause DIIPM malfunction (turns ON), so DC-link voltage need to turn on after control supply turning on. (Avoid inputting ON-signals to DIIPM before the control supply coming up to 13.5V)
4-UV trip level (P, N)	UV function becomes active and output Fo (N-side only). Even if control signals are applied, IGBT does not work
UV trip level-13.5V(N),13.0V(P)	IGBT can work. However, conducting loss and switching loss will increase, and result extra temperature rise at this state.
13.5-16.5V (N), 13.0-18.5V (P)	Recommended conditions. (Normal operation)
16.5-20V (N),18.5-20V (P)	IGBT works. However, switching speed becomes fast and saturation current becomes large at this state, increasing SC broken risk.
20V- (P, N)	Over maximum voltage rating. The control circuit will be destroyed.

Ripple Voltage Limitation of Control Supply

If high frequency precipitous noise is superimposed to the control supply line, IC malfunction might happen and cause DIIPM erroneous operation. To avoid such problem happens, line ripple voltage should meet the following specifications:

$$dV/dt \leq \pm 1V/\mu s, \quad V_{\text{ripple}} \leq 2V_{\text{p-p}}$$

N-side UV Protection Sequence

- a1. Control supply voltage V_D exceeds under voltage reset level (UV_{Dr}), but IGBT turns ON when inputting next ON signal ($L \rightarrow H$). (IGBT of each phase can return to normal state by inputting ON signal to each phase.)
- a2. Normal operation: IGBT turn on and carry current.
- a3. V_D level drops to under voltage trip level. (UV_{Dt}).
- a4. All N-side IGBTs turn OFF in spite of control input condition.
- a5. Fo outputs for the period determined by the capacitance C_{FO} , but output is extended during V_D keeps below UV_{Dr} .
- a6. V_D level reaches UV_{Dr} .
- a7. Normal operation: IGBT ON and carry current.

 


Fig.2-8 Timing chart of N-side UV protection

P-side UV Protection Sequence

- b1. Control supply voltage V_{DB} rises. After the voltage reaches under voltage reset level UV_{DBr} , IGBT can turn on when inputting next ON signal ($L \rightarrow H$).
- b2. Normal operation: IGBT ON and outputs current.
- b3. V_{DB} level drops to under voltage trip level (UV_{DBt}).
- b4. IGBT of corresponding phase only turns OFF in spite of control input signal level, but there is no F_o signal output.
- b5. V_{DB} level reaches UV_{DBr} .
- b6. Normal operation: IGBT ON and carry current.

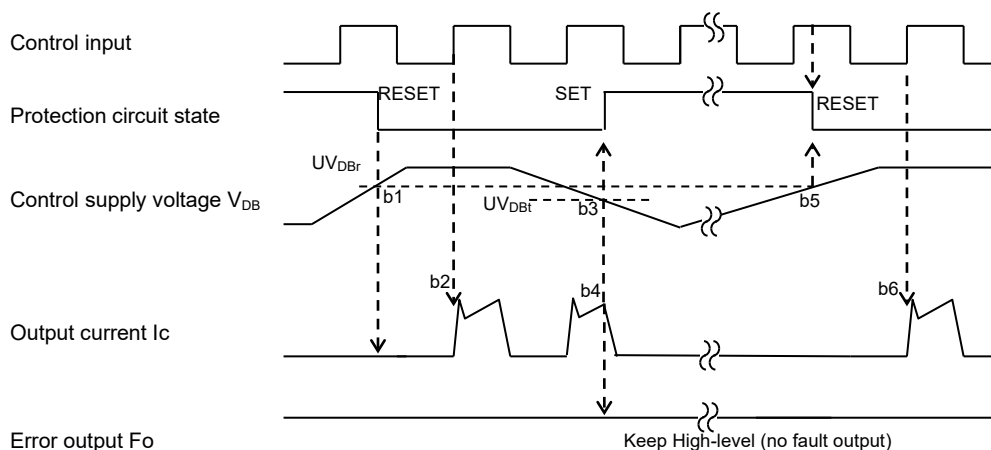


Fig.2-9 Timing Chart of P-side UV protection

2.2.3 Temperature Output Function

This function measures the temperature of control LVIC by built in temperature detecting circuit on LVIC. The heat generated at IGBT and FWDi transfers to LVIC through mold package and inner and outer heat sink. So that LVIC temperature cannot respond to rapid temperature change of power chips effectively. (e.g. motor lock, short current) It is recommended to use this function for protecting from excessive temperature rise by such cooling system down and continuance of overload operation. (Replacement from the thermistor which has been set on outer heat sink currently)

Also DIIPM cannot shutdown IGBT and output fault signal automatically when temperature rises excessively. When temperature exceeds the defined protect level, controller (MCU) should stop the DIIPM.

(1) V_{OT} terminal circuit and outer additional circuit

V_{OT} output circuit, which is described in Fig.2-10, is the output of OP amplifier circuit. The current capability of V_{OT} output is described as Table 2-12. Refer Fig.2-14 about output characteristics.

Table 2-12 Output capability
($T_c = -30^\circ\text{C} \sim 125^\circ\text{C}$)

	min.
Source	1.7mA
Sink	0.1mA

Source : Current flow from V_{OT} to outside.

Sink : Current flow from outside to V_{OT} .

 


Fig.2-10 Inner circuit of V_{OT} terminal

- In the case of detecting lower temperature than room temperature

It is recommended to insert 5.1k Ω pull down resistor for getting linear output characteristics at lower temperature than room temperature. When the pull down resistor is inserted between V_{OT} and V_{NC} (control GND), the extra current calculated by V_{OT} output voltage / pull down resistance flows as LVIC circuit current continuously. In the case of only using V_{OT} for detecting higher temperature than room temperature, it isn't necessary to insert the pull down resistor.

 


Fig.2-11 V_{OT} output circuit in the case of detecting low temperature

- In the case of using with low voltage controller(MCU)

In the case that V_{OT} output will be input to a low voltage controller (e.g. 3.3V MCU), V_{OT} output might exceed control supply voltage 3.3V when temperature rises excessively. If system uses low voltage controller, it is recommended to insert a clamp Di between control supply of the controller and this output for preventing over voltage.

 


Fig.2-12 V_{OT} output circuit in the case of using with low voltage controller

And if it is needed to set the trip level of V_{OT} output to the control supply voltage (e.g. 3.3V) or more, there is the method of dividing the V_{OT} output by resistance voltage divider circuit and then inputting to A/D converter on MCU (Fig.2-13). In that case, sum of the resistances of divider circuit should be 5.1k Ω . About the necessity of clamp diode, we consider that the divided output will not exceed the supply voltage of controller generally, so it will be unnecessary to insert the clamp diode. But it should be judged by the divided output level finally.

 
 


Fig.2-13 V_{OT} output circuit in the case with high protection level

(2) V_{OT} output characteristics

 
The characteristics of V_{OT} output vs. LVIC temperature is described as Fig.2-14. Please handle the following characteristics as reference data to set over temperature protection. These curves are based on theoretical designed value excluding specified value in the target specification.

Fig.2-14 V_{OT} output vs. LVIC temperature

(3) How to use V_{OT} output

As mentioned above, the heat of power chips transfers to LVIC through the package and heat sink, and the relationship between LVIC temperature: $T_{ic}(=V_{OT}$ output), case temperature: T_c (measuring point is defined on the datasheet), and junction temperature: T_j depend on the system cooling condition, heat sink, control strategy, etc.

For example, the evaluation result about the relationship between IGBT loss and these temperature is described as Fig.2-15. This relationship may be different due to the cooling conditions. So when setting the threshold temperature for protection, it is necessary to get the relationship between them on your real system and consider the protection temperature keeps $T_j \leq 150^\circ\text{C}$.

Fig.2-15 IGBT loss vs. T_j , T_c , T_{ic} (Typical) ($T_a=80^\circ\text{C}$)

Procedure about setting the protection level by using Fig.2-15 is described as below.



Table 2-13 Procedure for setting protection level

	Procedure	Setting value example
1)	Set the protection T_j temperature	Set T_j to 130°C as protection level.
2)	Get LVIC temperature T_{ic} that matches to above T_j of the protection level from the relationship of T_j - T_{ic} in Fig.2-16.	$T_{ic}=87.5^\circ\text{C}$ (@ $T_j=130^\circ\text{C}$)
3)	Get V_{OT} value from the V_{OT} output characteristics in Fig.2-17 and the T_{ic} value which was obtained at 2).	$V_{OT}=2.70\text{V}$ (@ $T_{ic}=87.5^\circ\text{C}$) is decided as the protection level.

As above procedure, the setting value for V_{OT} output is decided to 2.70V. But V_{OT} output has some data spread, so it is important to confirm whether the protection temperature fluctuation of T_j is not $T_j > 150^\circ\text{C}$ due to the data spread of V_{OT} output. Procedure about the confirmation of temperature fluctuation is described in Table 2-14.

Table 2-14 Procedure for confirmation of temperature fluctuation

	Procedure	Confirmation example
4)	Confirm the region of T_{ic} fluctuation at above V_{OT} from Fig.2-17.	$T_{ic}=82^\circ\text{C} \sim 94^\circ\text{C}$ (@ $V_{OT}=2.70\text{V}$)
5)	Confirm the region of T_j fluctuation at above region of T_{ic} from Fig.2-16.	$T_j=106^\circ\text{C} \sim 147^\circ\text{C}$ ($\leq 150^\circ\text{C}$, No problem) In this case, fluctuation of T_c is $T_c=90^\circ\text{C} \sim 111^\circ\text{C}$

  Fig.2-16 Relationship of T_j , T_c , T_{ic} (Enlarged graph of Fig.2-15)Fig.2-17 V_{OT} output vs. LVIC temperature (Enlarged graph of Fig.2-14)

The relationship between T_{ic} , T_c (measuring) and T_j (calculated by loss) depends on the system cooling condition and control strategy, and so on. So please evaluate about these temperature relationship on your real system when considering the protection level.

If necessary, it is available to prepare the sample with the individual data of V_{OT} vs. LVIC temperature.

2.3 Package Outlines

2.3.1 Outline Drawing

 


Fig.2-18 Outline drawing

2.3.2 Power Chip Position

Fig.2-19 indicates the center position of the each power chips.
(This figure is the view from laser marked side.)

 


Fig.2-19 Power chip position

2.3.3 Marking Position

The laser marking specification is described in Fig.2-20.
Company name, Country of origin, Type name, Lot number, and 2D code are marked in the upper side of module.

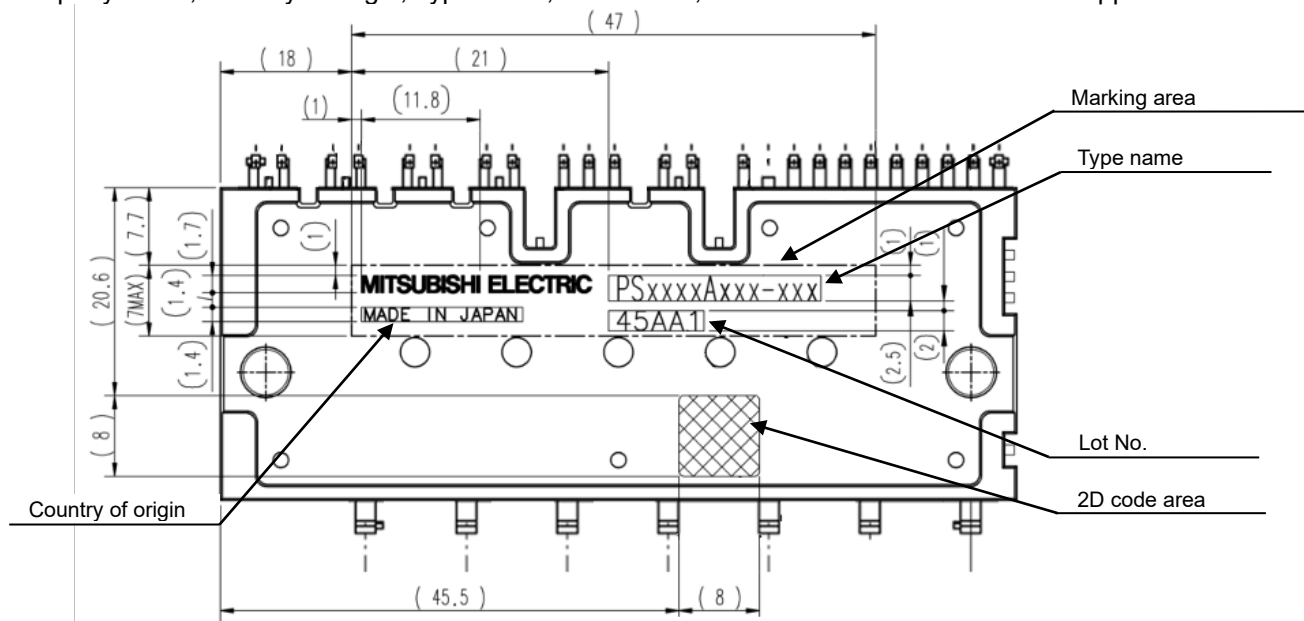


Fig.2-20 Laser marking view

The Lot number indicates production year, month, running number and country of origin.
The detailed is described as below.

(Example) 0 5 AA1

- Running number
- Product month (however O: October, N: November, D: December)
- Last figure of Product year (e.g. 2020)

2.3.4 Terminal Description

Table 2-15 Terminal description

No.	Name	Description
1	U _P	U-phase P-side control input terminal
3	V _{P1}	U-phase P-side control supply positive terminal
4	V _{UFB}	U-phase P-side drive supply positive terminal
6	V _{UFS}	U-phase P-side drive supply GND terminal
7	V _P	V-phase P-side control input terminal
9	V _{P1}	V-phase P-side control supply positive terminal
10	V _{VFB}	V-phase P-side drive supply positive terminal
12	V _{VFS}	V-phase P-side drive supply GND terminal
13	W _P	W-phase P-side control input terminal
14	V _{P1}	W-phase P-side control supply positive terminal
15	V _{PC}	P-side control supply GND terminal
16	V _{WFB}	W-phase P-side drive supply positive terminal
18	V _{WFS}	W-phase P-side drive supply GND terminal
19	V _{SC}	Sense current detecting terminal
21	V _{N1}	N-side control supply positive terminal
22	V _{NC}	N-side control supply GND terminal
23	V _{OT}	LVIC temperature output terminal
24	CIN	SC trip voltage detect terminal
25	CFO	Fault pulse output width set terminal
26	F _O	Fault signal output terminal
27	U _N	U-phase N-side control input terminal
28	V _N	V-phase N-side control input terminal
29	W _N	W-phase N-side control input terminal
34	NW	W-phase N-side IGBT emitter terminal
35	NV	V-phase N-side IGBT emitter terminal
36	NU	U-phase N-side IGBT emitter terminal
37	W	W-phase output terminal
38	V	V-phase output terminal
39	U	U-phase output terminal
40	P	Inverter DC-link positive terminal

No.	Name	Description
2	V _{PC}	Internal use (Dummy pin) Don't connect all dummy pins to any other terminals or PCB pattern. (Leave no connect)
5	U _{PG}	
8	V _{PC}	
11	V _{PG}	
17	W _{PG}	
20	V _{NG}	
30	V _{NC}	
31	W _{NG}	
32	V _{SC}	
33	NW	
41	V _{PC}	
42	U _{NG}	

600V LARGE DIIPM Ver.6 Series APPLICATION NOTE

Table 2-16 Detailed description of input and output terminals

Item	Symbol	Description
P-side drive supply positive terminal P-side drive supply GND terminal	V_{UFB} - V_{UFS} V_{VFB} - V_{VFS} V_{WFB} - V_{WFS}	<ul style="list-style-type: none"> Drive supply terminals for P-side IGBTs. Abnormal operation might happen if the V_D supply is not aptly stabilized or has insufficient current capability. In order to prevent malfunction caused by such unstability as well as noise and ripple in supply voltage, a bypass capacitor with favorable frequency and temperature characteristics should be mounted very closely to each pair of these terminals. Inserting a Zener diode (24V/1W) between each pair of control supply terminals is helpful to prevent control IC from surge destruction.
P-side control supply terminal N-side control supply terminal	V_{P1} V_{N1}	<ul style="list-style-type: none"> Control supply terminals for the built-in HVIC and LVIC. In order to prevent malfunction caused by noise and ripple in the supply voltage, a bypass capacitor with favorable frequency characteristics should be mounted very closely to these terminals. Carefully design the supply so that the voltage ripple caused by noise or by system operation is within the specified minimum limitation. It is recommended to insert a Zener diode (24V/1W) between each pair of control supply terminals to prevent surge destruction.
N-side control GND terminal	V_{PC} V_{NC}	<ul style="list-style-type: none"> Control ground terminal for the built-in HVIC and LVIC. Ensure that line current of the power circuit does not flow through this terminal in order to avoid noise influences.
Control input terminal	U_P, V_P, W_P U_N, V_N, W_N	<ul style="list-style-type: none"> Control signal input terminals. Voltage input type. These are internally connected to Schmitt trigger circuit. The wiring of each input should be as short as possible to protect the DIIPM from noise interference. Use RC coupling in case of signal oscillation.(Pay attention to threshold voltage of input terminal, because input circuit has pull down resistor (min 3.3kΩ))
Sense current detect terminal	V_{SC}	<ul style="list-style-type: none"> The sense current split at N-side IGBT flows out from this terminal. For SC protection, connect predefined resistor here.
Short-circuit trip voltage detecting terminal	CIN	<ul style="list-style-type: none"> Input the potential of V_{SC} terminal (with sense resistor) to CIN terminal for SC protection through RC filter (for the noise immunity). The time constant of RC filter is recommended to be up to 2μs.
Fault signal output terminal	F_O	<ul style="list-style-type: none"> Fault signal output terminal for N-side abnormal state(SC or UV). This output is open drain type. It is recommended to pull up F_O signal line to the 5V supply by 10kΩ when F_O signal is input to MCU directly (Check whether the V_{FO} satisfies the threshold level of input of MCU when selecting resistance). In the case of directly driving opto coupler by F_O output it is needed to set the pull-up resistance so that I_{FO} becomes under 5mA(maximum rating). And pulled up to 15V supply is recommended. (V_{FO} increases in proportion to increasing I_{FO}.)
Fault pulse output width setting terminal	CFO	<ul style="list-style-type: none"> The terminal is for setting the fault pulse output width. An external capacitor should be connected between this terminal and V_{NC}. When 22nF capacitor is connected, then the F_O pulse width becomes 2.4ms. $C_{FO} = t_{FO} \times 9.1 \times 10^{-6}$ (F)
Temperature output terminal	V_{OT}	<ul style="list-style-type: none"> LVIC temperature is output by analog signal. It is output of OP amplifier internally. It is recommended to connect 5.1kΩ pulldown resistor if output linearity is necessary under room temperature.
Inverter DC-link positive terminal	P	<ul style="list-style-type: none"> DC-link positive power supply terminal. Internally connected to the collectors of all P-side IGBTs. To suppress surge voltage caused by DC-link wiring or PCB pattern inductance, smoothing capacitor should be inserted very closely to the P and N terminal. It is also effective to add small film capacitor with good frequency characteristics.
Inverter DC-link negative terminal	NU, NV, NW	<ul style="list-style-type: none"> Open emitter terminal of each N-side IGBT If usage of common emitter is needed, connect these terminals together at the point as close from the package as possible.
Inverter power output terminal	U, V, W	<ul style="list-style-type: none"> Inverter output terminals for connection to inverter load (e.g. AC motor). Each terminal is internally connected to the intermediate point of the corresponding IGBT half bridge arm.

Note: Use oscilloscope to check voltage waveform of each power supply terminals and P&N terminals, the time division of OSC should be set to about 1 μ s/div. Please ensure the voltage (including surge) not exceed the specified limitation.

2.4 Mounting Method

This section shows the electric spacing and mounting precautions.

2.4.1 Electric Spacing

The electric spacing specification is shown in Table 2-17

Table 2-17 Minimum insulation distance

	Clearance (mm)	Creepage (mm)
Between live power terminals with high potential	7.1	7.8
Between live control terminals with high potential	3.1	5.6
Between terminals and heat sink	3.7	5.6

2.4.2 Mounting Method and Precautions

When installing the module to the heat sink, excessive or uneven fastening force might apply stress to inside chips. Then it will lead to a broken or degradation of the chips or insulation structure. The recommended fastening procedure is shown in Fig.2-21. When fastening, it is necessary to use the torque wrench and fasten up to the specified torque. And pay attention to the foreign particle on the contact surface between the module and the heat sink. Even if the fixing of heatsink was done by proper procedure and condition, there is a possibility of damaging the package because of tightening by unexpected excessive torque or tucking particle. For ensuring safety it is recommended to conduct the confirmation test(e.g. insulation inspection) on the final product after fixing the DIIPM with the heatsink.

 


Fig.2-21 Recommended screw fastening order

Temporary fastening
(1)→(2)

Permanent fastening
(1)→(2)

Note: Generally, the temporary fastening torque is set to 20-30% of the maximum torque rating.
Not care the order of fastening (1) or (2), but need to fasten alternately.

Table 2-18 Mounting torque and heat sink flatness specifications

Item	Condition	Min.	Typ.	Max.	Unit
Mounting torque	Recommended 1.18N·m, Screw : M4	0.98	1.18	1.47	N·m
Flatness of outer heat sink	Refer Fig.2-22	-50	-	+100	μm

 


Fig.2-22 Measurement point of heat sink flatness

In order to get effective heat dissipation, it is necessary to keep the contact area as large as possible to minimize the contact thermal resistance. Regarding the heat sink flatness (warp, concavity and convexity) on the module installation surface, the surface finishing-treatment should be within Rz12.

Evenly apply thermally conductive grease with 100μ-200μm thickness over the contact surface between the module and the heat sink, which is also useful for preventing corrosion. The contacting thermal resistance between DIIPM case and heat sink $R_{th(c-f)}$ is determined by the thickness and the thermal conductivity of the applied grease. For reference, $R_{th(c-f)}$ is about 0.2K/W (per 1/6 module, grease thickness: 20μm, thermal conductivity: 1.0W/m·k). When

600V LARGE DIIPM Ver.6 Series APPLICATION NOTE

applying grease and fixing heat sink, pay attention not to take air into grease. It might lead to make contact thermal resistance worse or loosen fixing in operation.

Pay attention to the selection of thermal conductive grease. The grease thickness after fixing the heatsink may increase due to the properties of the grease (contained filler diameter, viscosity, amount of application and so on). And it may cause increase of contact thermal resistance or package crack. Please contact thermal conductive grease manufacturer for its detailed characteristics.

2.4.3 Soldering Conditions

The recommended soldering condition is mentioned as below.

(Note: The reflow soldering cannot be recommended for DIIPM.)

(1) Flow (wave) Soldering

DIIPM is tested on the condition described in Table 2-19 about the soldering thermostability, so the recommended conditions for flow (wave) soldering are soldering temperature is up to 265°C and the immersion time is within 11s. However, the condition might need some adjustment based on flow condition of solder, the speed of the conveyer, and the land pattern and the through hole shape on the PCB, etc.

It is necessary to confirm whether it is appropriate or not for your real PCB finally.

Table 2-19 Reliability test specification

Item	Condition
Soldering Thermostability	260±5°C, 10±1s

(2) Hand soldering

Since the temperature impressed upon the DIIPM may changes based on the soldering iron types (wattages, shape of soldering tip, etc.) and the land pattern on PCB, we cannot suggest the recommended temperature condition for hand soldering.

As a general requirement of the temperature profile for hand soldering, the temperature of the root of the DIIPM terminal should be kept lower than 150°C for considering glass transition temperature (T_g) of the package molding resin and the thermal withstand capability of internal chips. Therefore, it is necessary to check the DIIPM terminal root temperature, solderability and so on in your real PCB, when configure the soldering temperature profile. (It is recommended to set the soldering time as short as possible.)

For reference, the evaluation example of hand soldering with 50W soldering iron is described as below.

[Evaluation method]

a. Sample: Large DIIPM Ver.6

b. Evaluation procedure

- Put the soldering tip of 50W iron (temperature set to 400°C) on the terminal within 1mm from the toe. (The lowest heat capacity terminal (=control terminal) is selected.)
- Measure the temperature rise of the terminal root part by the thermocouple installed on the terminal root.

 


Fig.2-23 Heating and measuring point

 


Fig.2-24 Temperature alteration of the terminal root (Example)

[NOTE] For soldering iron, it is recommended to select one for semiconductor soldering (12~24V low voltage type, and the earthed iron tip) and with temperature adjustment function.

CHAPTER 3 SYSTEM APPLICATION HIGHLIGHT

3.1 Application Guidance

This chapter states usage and interface circuit design hints.

3.1.1 System Connection

C1: Electrolytic type with good temperature and frequency characteristics

Note: the capacitance also depends on the PWM control strategy of the application system

C2: 0.01 μ F ceramic capacitor with good temperature, frequency and DC bias characteristics

C3: 0.1 μ -0.22 μ F Film capacitor (for snubber)

D1: Zener diode 24V/1W for surge absorber

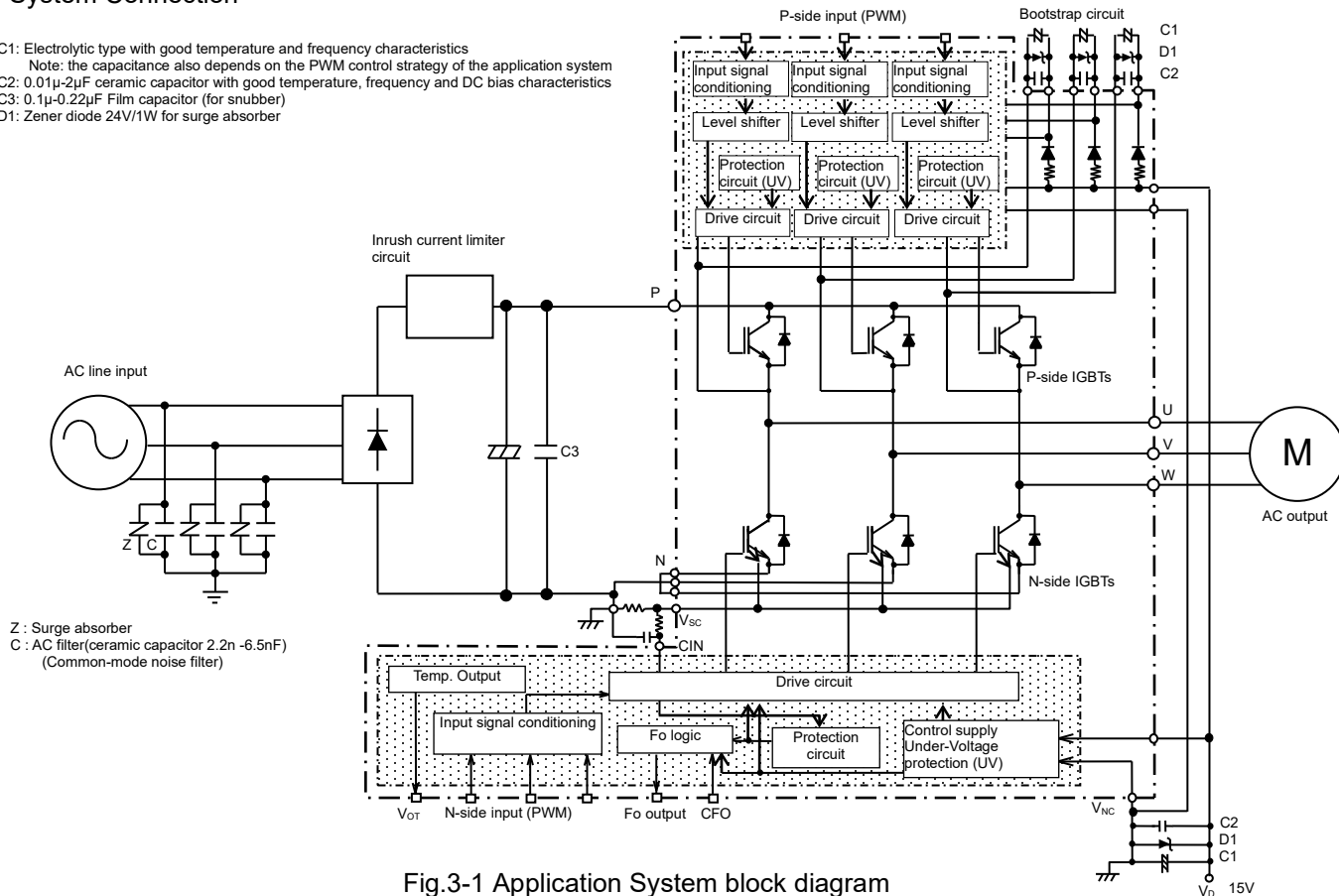


Fig.3-1 Application System block diagram

Fig.3-2 shows a typical application circuit of connecting with MCU or DSP directly.

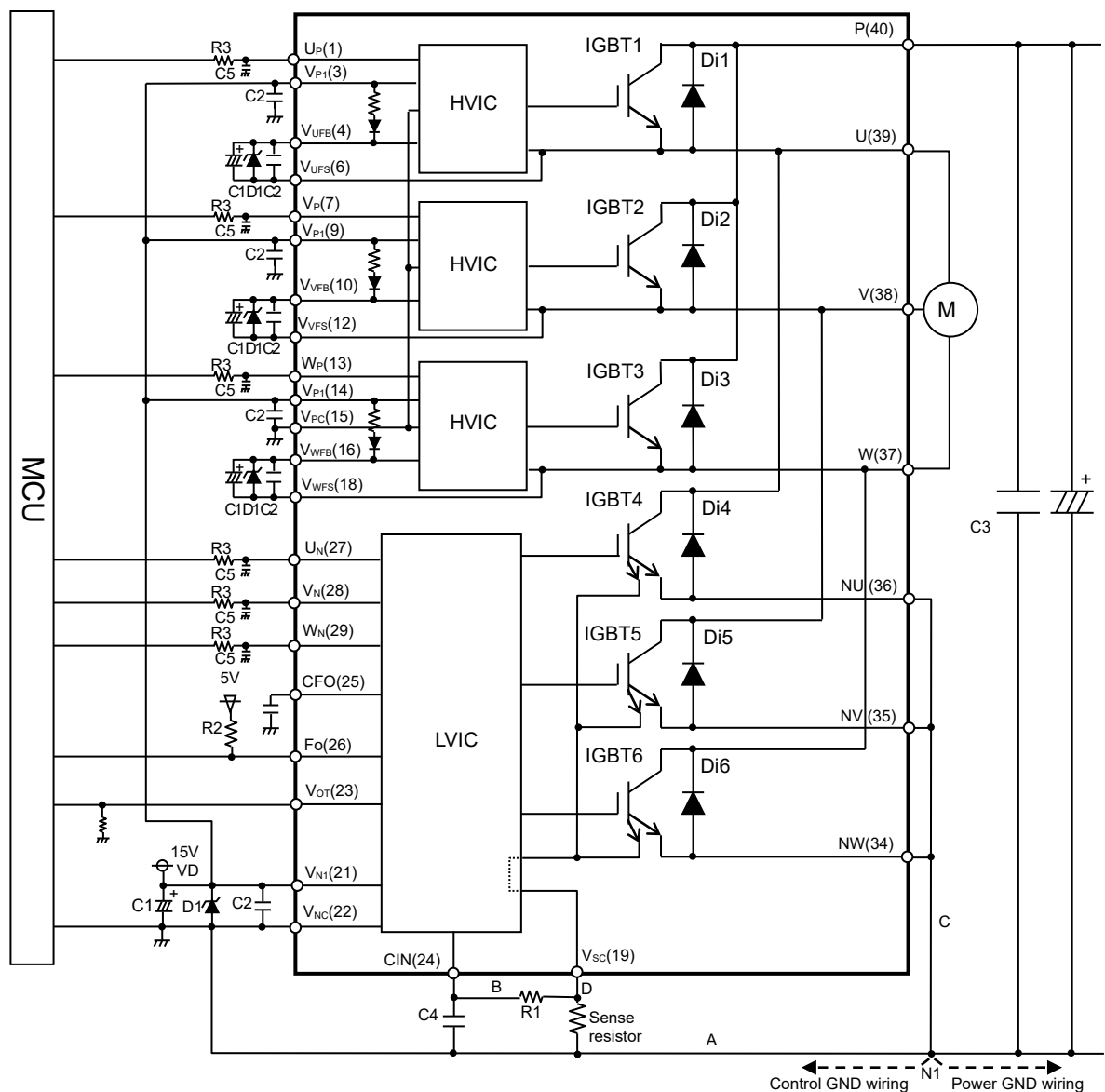


Fig.3-2 Interface circuit example (Direct coupling)

- 1 :If control GND and power GND are patterned by common wiring, it may cause malfunction by fluctuation of power GND level. It is recommended to connect control GND and power GND at only a N1 point at which NU, NV, NW are connected to power GND line.
- 2 :It is recommended to insert a Zener diode D1 (24V/1W) between each pair of control supply terminals to prevent surge destruction.
- 3 :To prevent surge destruction, the wiring between the smoothing capacitor and the P, N1 terminals should be as short as possible. Generally inserting a $0.1\mu\sim 0.22\mu\text{F}$ snubber capacitor C3 between the P-N1 terminals is recommended.
- 4 :R1, C4 of RC filter for preventing protection circuit malfunction is recommended to select tight tolerance, temp-compensated type. The time constant $R1C4$ should be set so that SC current is shut down within $2\mu\text{s}$. ($1.5\mu\sim 2\mu\text{s}$ is general value.) SC interrupting time might vary with the wiring pattern, so the enough evaluation on the real system is recommended. If R1 is too small, it may leads to delay of protection. So R1 should be min. 10 times larger resistance than Rs. (100 times is recommended.)
- 5 :To prevent erroneous operation, the wiring of A, B, C should be as short as possible.
- 6 :For sense resistor, the variation within 1%(including temperature characteristics), low inductance type is recommended. And the over 0.03W is recommended, but it is necessary to evaluate in your real system finally.
- 7 :To prevent erroneous SC protection, the wiring from V_{SC} terminal to CIN filter should be divided at the point D that is close to the terminal of sense resistor. And the wiring should be patterned as short as possible.
- 8 :All capacitors should be mounted as close to the terminals of the DIPIPM as possible. (C1: good temperature, frequency characteristic electrolytic type, and C2: $0.01\mu\sim 2.0\mu\text{F}$, good temperature, frequency and DC bias characteristic ceramic type are recommended.)
- 9 :Input drive is High-active type. There is a min. $3.3\text{k}\Omega$ pull-down resistor in the input circuit of IC. To prevent malfunction, the wiring of each input should be as short as possible. And it is recommended to insert RC filter (e.g. $R3=100\Omega$ and $C5=1000\text{pF}$) and confirm the input signal level to meet the turn-on and turn-off threshold voltage. Thanks to HVIC inside the module, direct coupling to MCU without any opto-coupler or transformer isolation is possible.
- 10 :Fo output is open drain type. Fo output will be max $0.95\text{V} (@I_{FO}=1\text{mA}, 25^\circ\text{C})$, so it should be pulled up to MCU or control power supply (e.g. 5V, 15V) by a resistor that makes I_{FO} up to 1mA. (In the case of pulled up to 5V, $10\text{k}\Omega$ is recommended.)
- 1 :Error signal output width (t_{FO}) can be set by the capacitor connected to C_{FO} terminal. $C_{FO}(\text{typ.}) = t_{FO} \times (9.1 \times 10^{-6}) (\text{F})$
- 2 :If high frequency noise superimposed to the control supply line, IC malfunction might happen and cause erroneous operation. To avoid such problem, voltage ripple of control supply line should meet $dV/dt \leq \pm 1\text{V}/\mu\text{s}$, $\text{Vripples} \leq 2\text{Vp-p}$.
- 3 :For DIPIPM, it isn't recommended to drive same load by parallel connection with other phase IGBT or other DIPIPM.

3.1.3 Interface Circuit (Opto-coupler Isolated Interface)

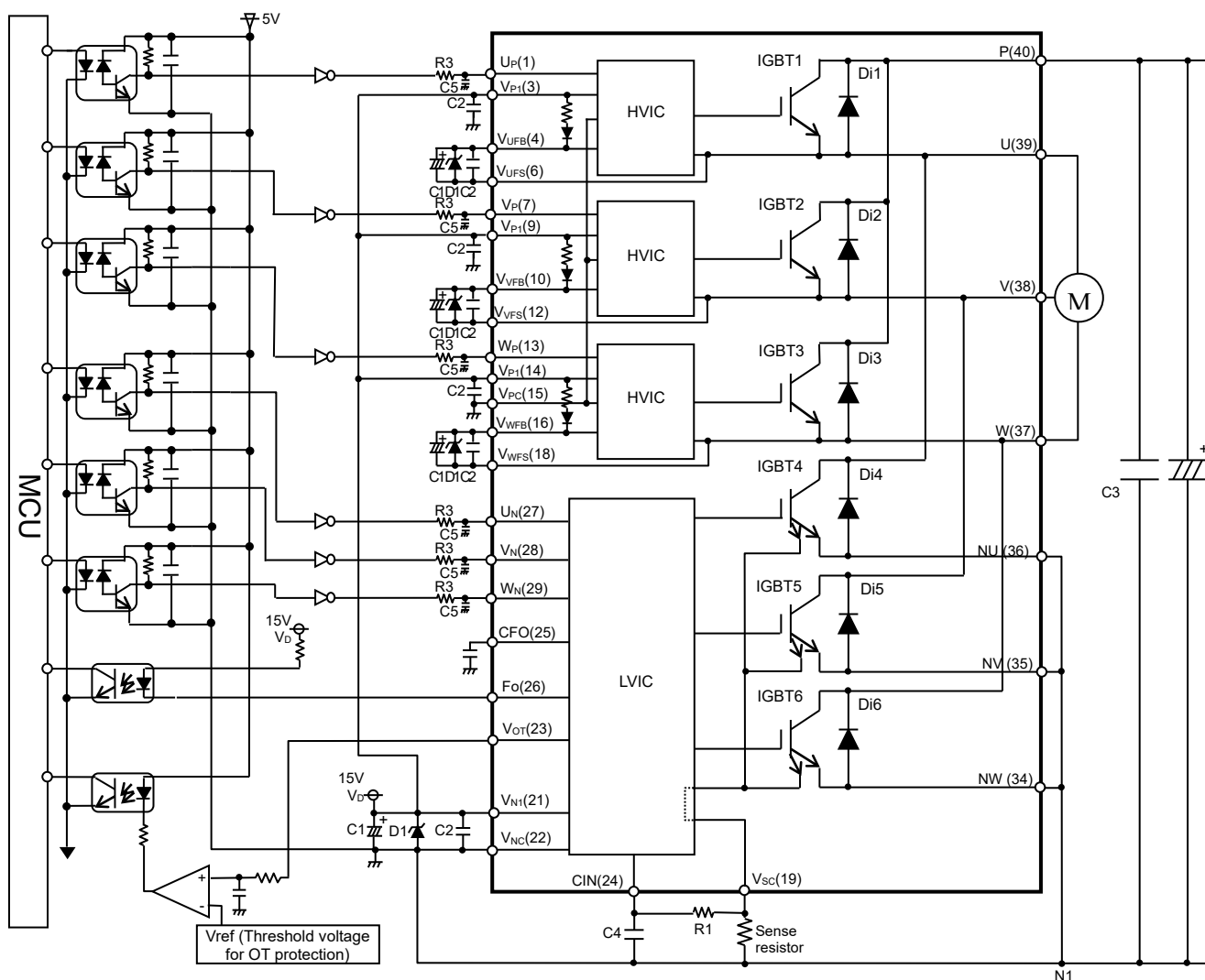


Fig.3-3 Interface circuit example with opto-coupler

Note:

- (1) High speed (high CMR) opto-coupler is recommended.
- (2) Set the current limiting resistance to make $I_{FO}=5\text{mA}$ or less when the opto-coupler is driven by F_O output directly. To assure $I_{FO}=5\text{mA}$, it will be needed to pull up to 15V supply since F_O output may be max $4.75\text{V} (@I_{FO}=5\text{mA}, 25^\circ\text{C})$.
- (3) To prevent malfunction, it is strongly recommended to insert RC filter (e.g. $R3=100\Omega$ and $C5=1000\text{pF}$) and confirm the input signal level to meet turn-on and turn-off threshold voltage.
- (4) About comparator circuit at V_{OT} output, it is recommended to design the input circuit with hysteresis because of preventing output chattering.

3.1.4 Circuits of Signal Input terminals and Fo Terminal

Input logic is high-active. A 3.3k Ω (min) pull-down resistor is built-in each input circuit of the DIIPM as shown in Fig.3-4, so external pull-down resistor is not needed.

This series have same package as 1200V large DIIPM Ver.4 series (PS22A7*) and 1200V large DIIPM Ver.6 series (PSS**SA2FT), however, they have different input threshold voltage. When using same PCB between these series, it needs to give attention to the difference.

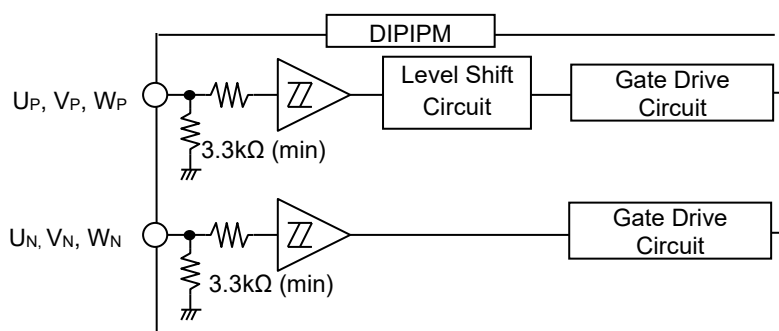


Fig.3-4 Internal structure of control input terminals

Table 3-1 Input threshold voltage ratings (T_j=25°C)

Item	Symbol	Condition	Min.	Typ.	Max.	Unit
Turn-on threshold voltage	V _{th(on)}	U _P , V _P , W _P -V _{PC}	-	2.1	2.6	V
Turn-off threshold voltage	V _{th(off)}	U _N , V _N , W _N -V _{NC}	0.8	-	-	

The wiring of each input should be patterned as short as possible and it is recommended to insert RC filter. There are limits for the minimum input pulse width in the DIIPM. DIIPM might make no response or delayed response, if the input pulse width (both on and off) is shorter than the specified value. (Refer Table 3-2)

 


Fig.3-5 Control input connection in the case of direct connection with MCU

Note: Design for input RC filter depends on the PWM control scheme used in the application and the wiring impedance of the printed circuit board. It is recommended to insert RC filter. (Time constant: over 100ns. e.g. 100 Ω , 1000pF)

DIIPM input signal interface integrates a 3.3k Ω (min.) pull-down resistor. Therefore, when using RC filter, be careful to satisfy the turn-on threshold voltage requirement.

Table 3-2 Allowable minimum input pulse width

	Symbol	Type Name	Minimum value	Unit
On signal	PWIN(on)	PSS50SA2F6	1.5	μs
		PSS75SA2F6		
Off signal	PWIN(off)	PSS50SA2F6	3.0	
		PSS75SA2F6		

- DIIPM might not make response if the input signal pulse width is less than PWIN(on).
- DIIPM might make no response or delayed response (P-side IGBT only) for input pulse width less than PWIN(off).
Over rated collector current (I_c) operation, DIIPM might make delayed response even if the input signal pulse width is more than PWIN(off).

Refer Fig.3-6 about delayed response.

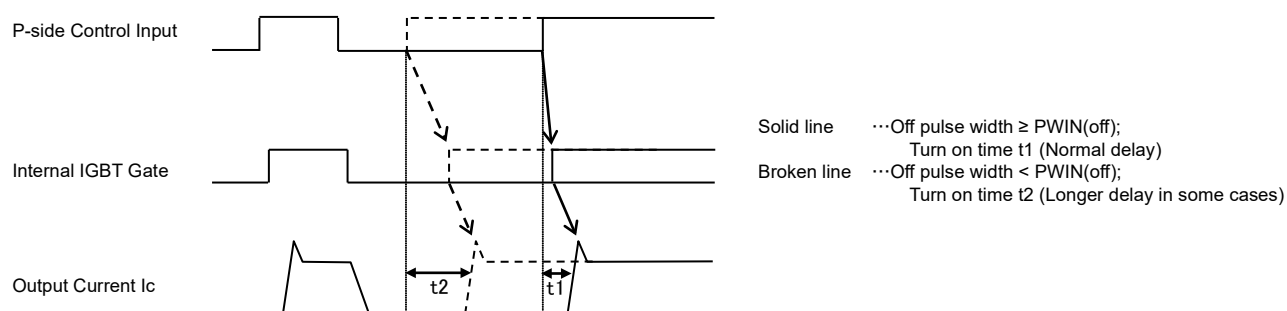


Fig.3-6 Delayed response with shorter input off (P-side only)

(2) Internal Circuit of Fo Terminal

F_O terminal is an open drain type. When F_O output is input into MCU(controller) directly, it is necessary to note the dependency of V_{FO} on I_{FO} (V_{FO}=max0.95V @I_{FO}=1mA, 25°C) and set pull up resistance so that F_O signal level fits to the input threshold voltage of MCU. In the case of pulling up to 5V supply, it is recommended to pull up by 10kΩ resistor.

When the opto-coupler is driven by F_O output directly, the maximum F_O sink current becomes 5mA or less. To assure I_{FO}=5mA, it will be needed to pull up to 15V supply since F_O output may be max 4.75V (@I_{FO}=5mA, 25°C).

If max 5mA coupler driving current is not enough, it is necessary to apply buffer circuit for increasing driving current.

Fig.3-7 shows the typical V-I characteristics of F_O terminal.

Table 3-3 Electric characteristics of F_O terminal

Item	Symbol	Condition	Min.	Typ.	Max.	Unit
Fault output voltage	V _{FOH}	V _{SC} =0V, F _O =10kΩ, 5V pulled-up	4.9	-	-	V
	V _{FOL}	V _{SC} =1V, F _O =1mA	-	-	0.95	V

 


Fig.3-7 F_O terminal typical V-I characteristics (V_D=15V, T_j=25°C)

3.1.5 Snubber Circuit

In order to prevent DIIPM from the surge destruction, the wiring length between the smoothing capacitor and DIIPM P-N terminals should be as short as possible. Also, a 0.1μ~0.22μF/630V snubber capacitor should be mounted to the position between P and the connect point of NU, NV and NW terminals as close as possible as Fig.3-8.

 


Fig.3-8 Recommended snubber circuit position

3.1.6 Influence of Wiring

Influence of pattern wiring around the sense resistor for SC protection and GND is shown below.

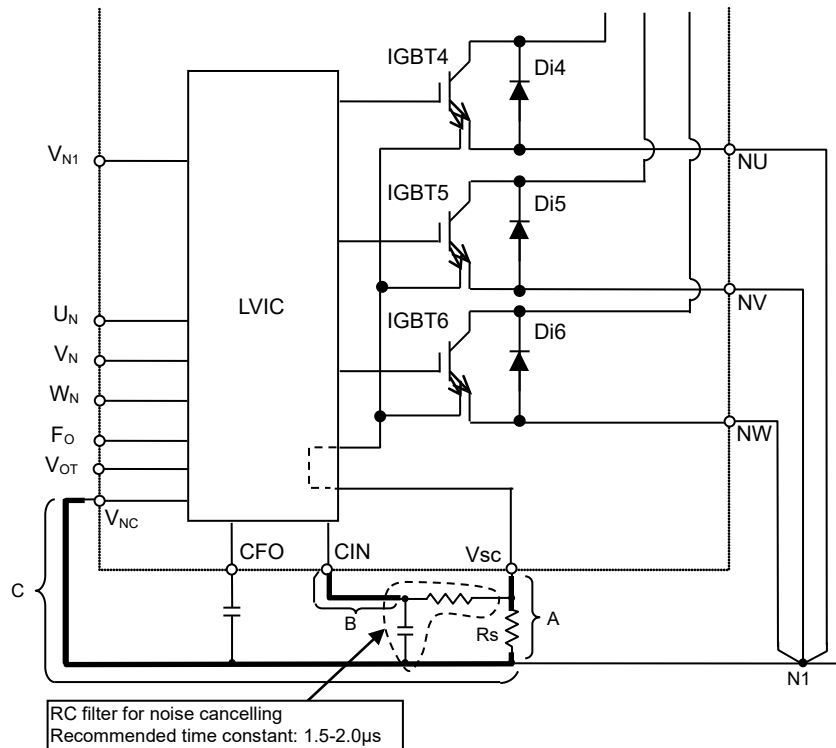


Fig.3-9 External protection circuit

(1) Influence of the part-A wiring

The part-A wiring affects SC protection level. SC protection works by judging the voltage of the CIN terminals. If part-A wiring is too long, extra surge voltage generated by the wiring inductance will lead to fluctuation of SC protection level. This wiring should be as short as possible for limiting the surge voltage.

(2) Influence of the part-B wiring pattern

RC filter is added to remove noise influence occurring on the sense resistor. Filter effect will drop down and noise will easily superimpose on the wiring, if part-B wiring (=after filtering part) is too long. Please install the RC filter near CIN, VNC terminals as close as possible.

(3) Influence of the part-C wiring pattern

Part-C wiring pattern gives influence to all the items described above, maximally shorten the GND wiring is expected. If control GND is connected to power GND by broad pattern, it may cause malfunction by power GND fluctuation. It is recommended to connect control GND and power GND at only a point at which NU, NV, NW are connected to power GND line.

3.1.7 Precaution for Wiring on PCB

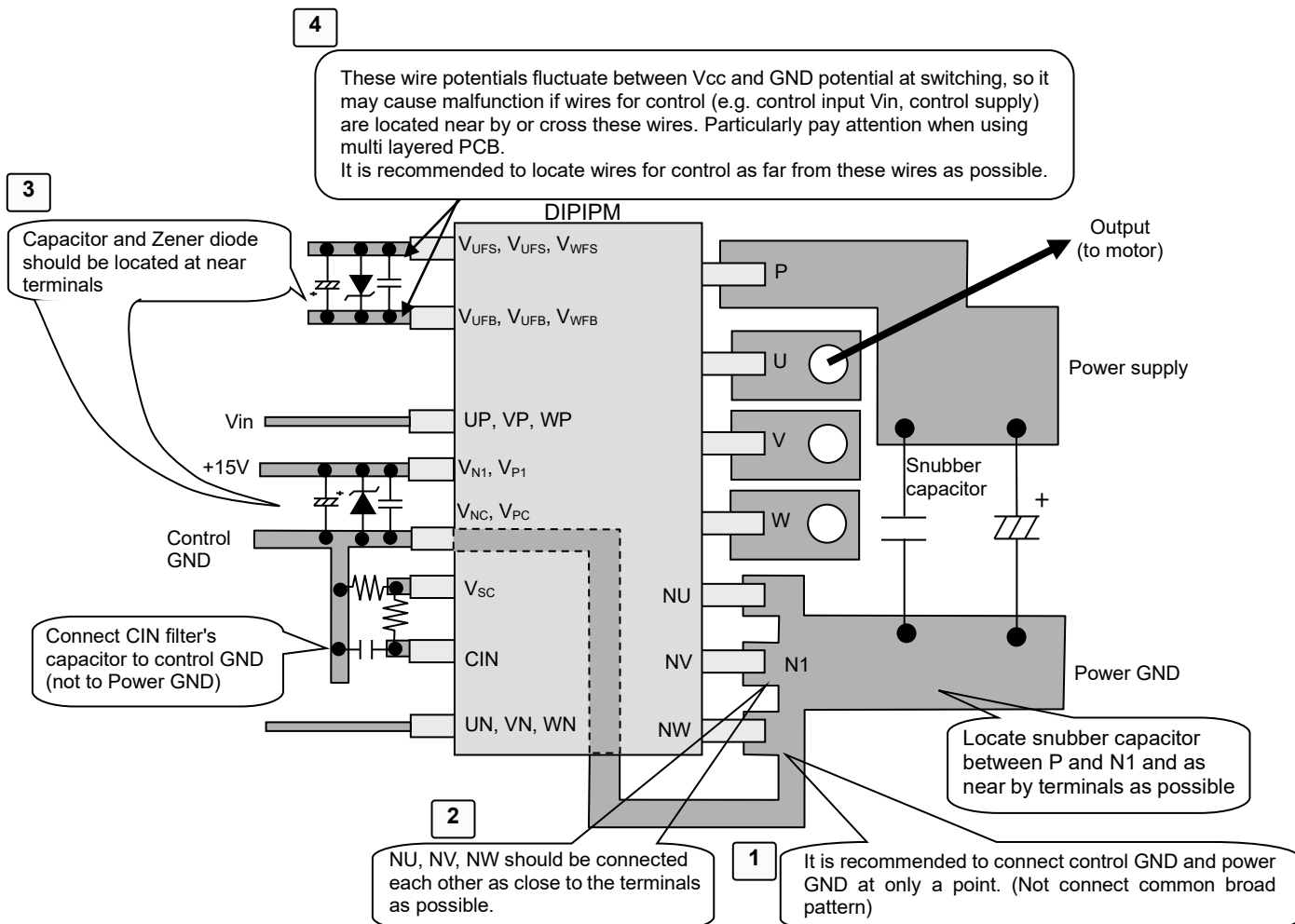


Fig.3-10 Precaution for wiring on PCB

The case example of trouble due to PCB pattern

	Case example	Matter of trouble
1	•Control GND pattern overlaps power GND pattern.	The surge, generated by the wiring pattern and di/dt of noncontiguous big current flows to power GND, transfers to control GND pattern. it causes the control GND level fluctuation, so that the input signal based on the control GND fluctuates too. Finally the arm short occurs.
	•Ground loop pattern exists.	Stray current flows to GND loop pattern, so that the control GND level and input signal level (based on the GND) fluctuates. Then the arm short occurs.
2	•Long pattern between NU, NV, NW terminals and N1	Long wiring pattern has big parasitic inductance and generates high surge when switching. This surge causes the matter as below. •HVIC malfunction due to VS voltage (output terminal potential) dropping excessively. •LVIC surge destruction
3	Capacitors or zener diodes are nothing or located far from the terminals.	IC surge destruction or malfunction occurs.
4	The input lines are located parallel and close to the floating supply lines for P-side drive.	Cross talk noise might be transferred through the capacitance between these floating supply lines and input lines to DIIPM. Then incorrect signals are input to DIIPM input, and arm short (short circuit) might occur.

3.1.8 SOA of DIIPM

The following describes the SOA (Safety Operating Area) of DIIPM.

V_{CES} : Maximum rating of IGBT collector-emitter voltage

V_{CC} : Supply voltage applied on P-N terminals

$V_{CC(surge)}$: The total amount of V_{CC} and the surge voltage generated by the wiring inductance and the DC-link capacitor.

$V_{CC(PROT)}$: DC-link voltage that DIIPM can protect itself.

 


Fig.3-11 SOA at switching mode

 


Fig.3-12 SOA at short-circuit mode

In case of switching

V_{CES} represents the maximum voltage rating (600V) of the IGBT. By subtracting the surge voltage (100V or less) generated by internal wiring inductance from V_{CES} is $V_{CC(surge)}$, that is 500V. Furthermore, by subtracting the surge voltage (50V or less) generated by the wiring inductor between DIIPM and DC-link capacitor from $V_{CC(surge)}$ derives V_{CC} , that is 450V.

In case of Short-circuit

V_{CES} represents the maximum voltage rating (600V) of the IGBT. By Subtracting the surge voltage (100V or less) generated by internal wiring inductor from V_{CES} is $V_{CC(surge)}$, that is, 500V. Furthermore, by subtracting the surge voltage (100V or less) generated by the wiring inductor between the DIIPM and the electrolytic capacitor from $V_{CC(surge)}$ derives V_{CC} , that is, 400V.

3.1.9 SCSOA

Fig.3-13 and Fig.3-14 show the typical SCSOA performance curves

Conditions: $V_{cc}=400V$, $T_j=150^{\circ}C$ at initial state, $V_{cc}(\text{surge})\leq 500V(\text{surge included})$, non-repetitive, 2m load.

In the case of PSS50SA2F6 (50A rating) it means DIIPM can shutdown maximum 490A(@ $V_D=16.5V$) short circuit current safely if IGBT turn on period is within 4.0 μs (typical).

Since the SCSOA operation area will vary with the control supply voltage, DC-link voltage, and etc, it is necessary to set time constant of RC filter with a margin.

 


Fig.3-13 PSS50SA2F6 typical SCSOA curve

 


Fig.3-14 PSS75SA2F6 typical SCSOA curve

3.1.10 Power Life Cycles

When DIIPM is in operation, repetitive temperature variation will happens on the IGBT junctions (ΔT_j). The amplitude and the times of the junction temperature variation affect the device lifetime.

Fig.3-15 shows the IGBT power cycle curve as a function of average junction temperature variation (ΔT_j).

(The curve is a regression curve based on 3 points of $\Delta T_j=46, 88, 98\text{K}$ with regarding to failure rate of 0.1%, 1% and 10%. These data are obtained from the reliability test of intermittent conducting operation)

 


Fig.3-15 Power cycle curve

3.2 Power Loss and Thermal Dissipation Calculation**3.2.1 Power Loss Simulation**

For calculating power loss and temperature rising, the power loss simulator "Melcosim" is prepared in our WEB site. This simulator can make the calculation of inverter loss and temperature rise easy.

The 'Melcosim' can be downloaded from <http://www.mitsubishielectric.com/semiconductors/>

Simple expressions for calculating average power loss are given below:

- Scope

The power loss calculation intends to provide users a way of selecting a matched power device for their VVVF inverter application. However, it is not expected to use for limit thermal dissipation design.

- Assumptions

- (1) PWM controlled VVVF inverter with sinusoidal output;
- (2) PWM signals are generated by the comparison of sine waveform and triangular waveform.
- (3) Duty amplitude of PWM signals varies between $\frac{1-D}{2} \sim \frac{1+D}{2}$ (%/100), (D: modulation depth).
- (4) Output current varies with $I_{cp} \cdot \sin x$ and it does not include ripple.
- (5) Power factor of load output current is $\cos \theta$, ideal inductive load is used for switching.

- Expressions Derivation

PWM signal duty is a function of phase angle x as $\frac{1+D \times \sin x}{2}$ which is equivalent to the output voltage variation. From the power factor $\cos \theta$, the output current and its corresponding PWM duty at any phase angle x can be obtained as below:

$$\begin{aligned} \text{Output current} &= I_{cp} \times \sin x \\ \text{PWM Duty} &= \frac{1 + D \times \sin(x + \theta)}{2} \end{aligned}$$

Then, $V_{CE(sat)}$ and V_{EC} at the phase x can be calculated by using a linear approximation:

$$\begin{aligned} V_{ce(sat)} &= V_{ce(sat)}(@ I_{cp} \times \sin x) \\ V_{ec} &= (-1) \times V_{ec}(@ I_{cp}(= I_{cp}) \times \sin x) \end{aligned}$$

Thus, the static loss of IGBT is given by:

$$\frac{1}{2\pi} \int_0^\pi (I_{cp} \times \sin x) \times V_{ce(sat)}(@ I_{cp} \times \sin x) \times \frac{1 + D \sin(x + \theta)}{2} \bullet dx$$

Similarly, the static loss of free-wheeling diode is given by:

$$\frac{1}{2\pi} \int_\pi^{2\pi} ((-1) \times I_{cp} \times \sin x) ((-1) \times V_{ec}(@ I_{cp} \times \sin x) \times \frac{1 + D \sin(x + \theta)}{2}) \bullet dx$$

On the other hand, the dynamic loss of IGBT, which does not depend on PWM duty, is given by:

$$\frac{1}{2\pi} \int_0^\pi (P_{sw(on)}(@ I_{cp} \times \sin x) + P_{sw(off)}(@ I_{cp} \times \sin x)) \times f_c \bullet dx$$

FWDi recovery characteristics can be approximated by the ideal curve shown in Fig.3-16, and its dynamic loss can be calculated by the following expression:

 


Fig.3-16 Ideal FWDi recovery characteristics curve

$$P_{sw} = \frac{I_{rr} \times V_{cc} \times trr}{4}$$

Recovery occurs only in the half cycle of the output current, thus the dynamic loss is calculated by:

$$\begin{aligned} & \frac{1}{2} \int_{\pi}^{2\pi} \frac{I_{rr}(@ I_{cp} \times \sin x) \times V_{cc} \times trr(@ I_{cp} \times \sin x)}{4} \times fc \cdot dx \\ &= \frac{1}{8} \int_{\rho}^{2\pi} I_{rr}(@ I_{cp} \times \sin x) \times V_{cc} \times trr(@ I_{cp} \times \sin x) \times fc \cdot dx \end{aligned}$$

- Attention of applying the power loss simulation for inverter designs
 - Divide the output current period into fine-steps and calculate the losses at each step based on the actual values of PWM duty, output current, $V_{CE(sat)}$, V_{EC} , and P_{sw} corresponding to the output current. The worst condition is most important.
 - PWM duty depends on the signal generating way.
 - The relationship between output current waveform or output current and PWM duty changes with the way of signal generating, load, and other various factors. Thus, calculation should be carried out on the basis of actual waveform data.
 - $V_{CE(sat)}$, V_{EC} and $P_{sw}(on, off)$ should be the values at $T_j=125^{\circ}\text{C}$.

3.2.2 Temperature Rise Considerations and Calculation Example

Fig.3-17 shows the typical characteristics of allowable motor rms current versus carrier frequency under the following inverter operating conditions based on power loss simulation results.

Conditions: $V_{CC}=300V$, $V_D=V_{DB}=15V$, $V_{CE(sat)}=Typ.$, $P.F=0.8$, Switching loss=Typ., $T_j=125^{\circ}C$, $T_c=100^{\circ}C$, $R_{th(j-c)}=Max.$, 3-phase PWM modulation, 60Hz sine waveform output

 


Fig.3-17 Effective current-carrier frequency characteristic

Fig.3-17 shows an example of estimating allowable inverter output rms current under different carrier frequency and permissible maximum operating temperature condition ($T_c=100^{\circ}C$ and $T_j=125^{\circ}C$). The results may change for different control strategy and motor types. Anyway please ensure that there is no large current over device rating flowing continuously.

The inverter loss can be calculated by the free power loss simulation software will be uploaded on the Mitsubishi Electric web site. (URL: <http://www.mitsubishielectric.com/semiconductors/>)

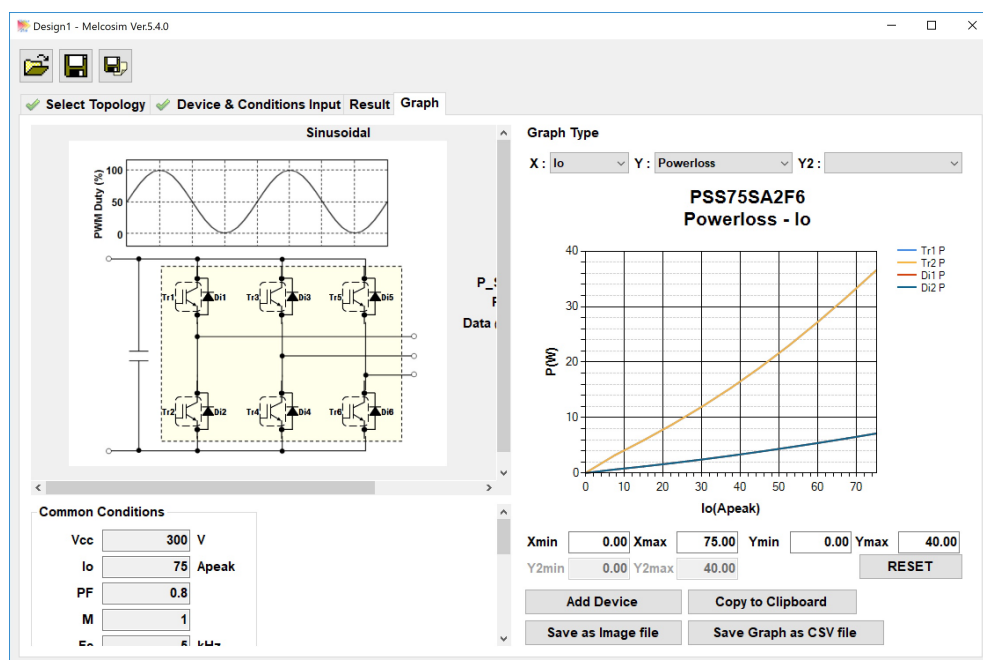


Fig.3-18 Loss simulator screen image

3.3 Noise and ESD Withstand Capability**3.3.1 Evaluation Circuit of Noise Withstand Capability**

DIIPM have been confirmed to be with over $\pm 2.0\text{kV}$ noise withstand capability by the noise evaluation under the conditions shown in Fig.3-19. However, noise withstand capability greatly depends on the test environment, the wiring patterns of control substrate, parts layout, and other factors, an additional confirmation on prototype is necessary.

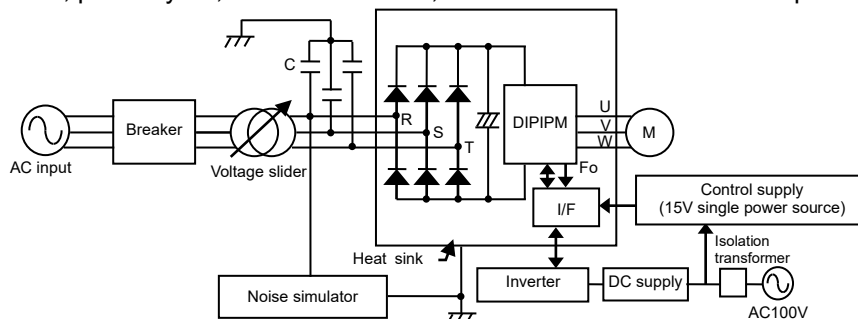


Fig.3-19 Noise withstand capability evaluation circuit

Note: C1: AC line common-mode filter 4700pF, PWM signals are input from microcomputer by using opto-couplers, 15V single power supply, Test is performed with IM

Test conditions

$V_{CC}=300\text{V}$, $V_D=15\text{V}$, $T_a=25^\circ\text{C}$, no load

Scheme of applying noise: From AC line (R, S, T), Period $T=16\text{ms}$, Pulse width $t_w=0.05\text{--}1\mu\text{s}$, input in random.

3.3.2 Countermeasures and Precautions

DIIPM improves noise withstand capabilities by means of reducing parts quantity, lowering internal wiring parasitic inductance, and reducing leakage current. But when the noise affects on the control terminals of DIIPM (due to no good wiring pattern on PCB), the short circuit or malfunction of SC protection may occur. In that case, the countermeasures are recommended.

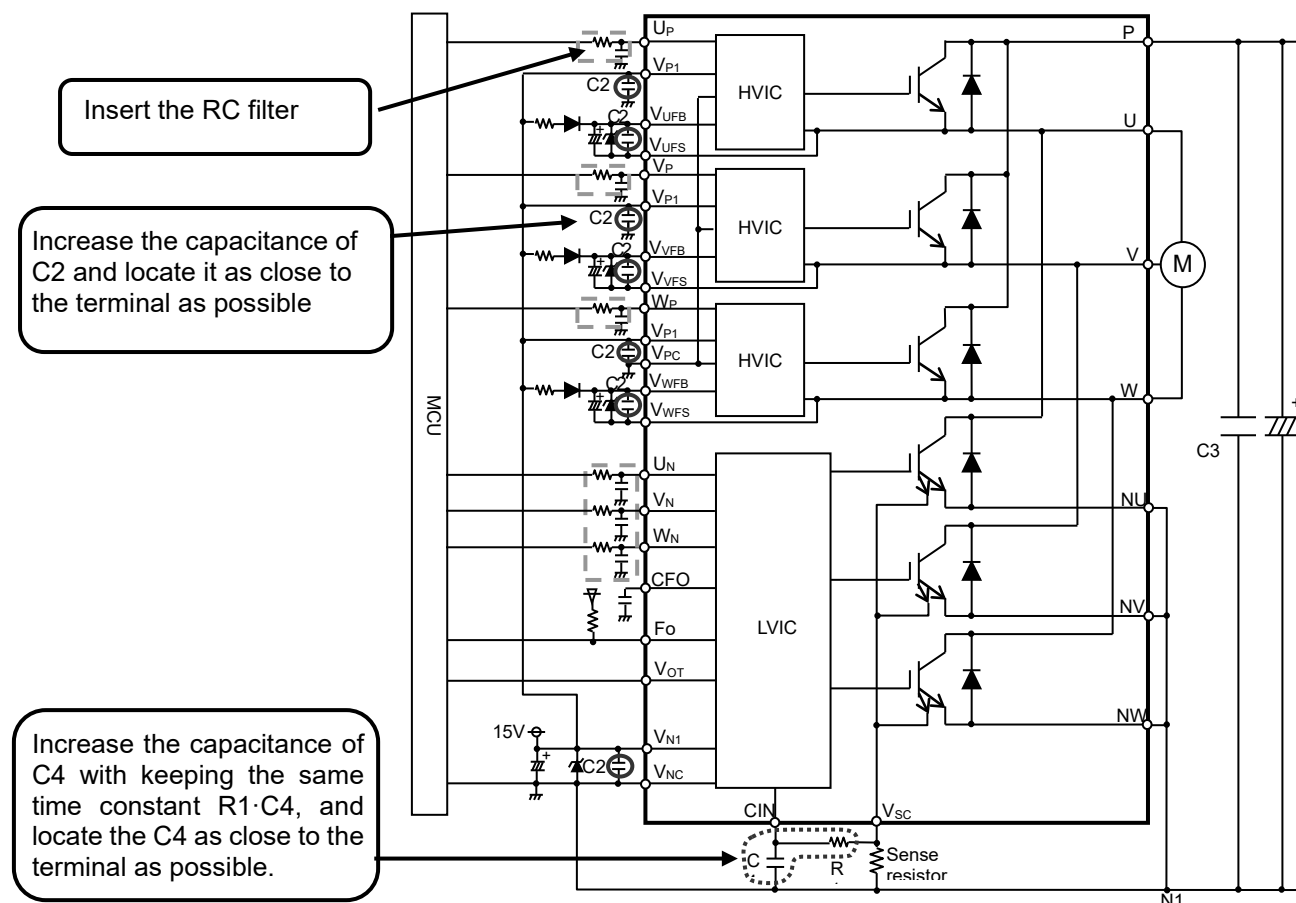
 
 


Fig.3-20 Example of countermeasures

3.3.3 Static Electricity Withstand Capability

DIIPM has been confirmed to be with typical $\pm 1\text{kV}$ or more withstand capability against static electricity from the following tests shown in Fig.3-21, 22. HBM method: $C=100\text{pF}$, $R=1.5\text{ k}\Omega$.

Fig.3-21 Surge test circuit example(V_{N1} terminal)Fig.3-22 Surge test circuit example(V_{P1} terminal)

CHAPTER 4 Bootstrap Circuit Operation

4.1 Bootstrap Circuit Operation

For three phase inverter circuit driving, normally four isolated control supplies (three for P-side driving and one for N-side driving) are necessary. But using floating control supply with bootstrap circuit can reduce the number of isolated control supplies from four to one (N-side control supply).

Bootstrap circuit consists of a bootstrap diode(BSD), a bootstrap capacitor(BSC) and a current limiting resistor.

It uses the BSC as a control supply for driving P-side IGBT. The BSC supplies gate charge when P-side IGBT turning ON and circuit current of logic circuit on P-side driving IC. (Fig.4-2) Since a capacitor is used as substitute for isolated supply, its supply capability is limited. This floating supply driving with bootstrap circuit is suitable for small supply current products like DIIPM.

Charge consumed by driving circuit is re-charged from N-side 15V control supply to BSC via current limiting resistor and BSD when voltage of output terminal (U, V or W) goes down to GND potential in inverter operation. But there is the possibility that enough charge doesn't perform due to the conditions such as switching sequence, capacitance of BSC, limiting resistance and so on. Deficient charge leads to low voltage of BSC and might work under voltage protection (UV). This situation makes the loss of P-side IGBT increase by low gate voltage or stop switching. So it is necessary to consider and evaluate enough for designing bootstrap circuit. For more detail information about driving by the bootstrap circuit, refer the DIIPM application note "*Bootstrap Circuit Design Manual*".

The built-in BSD characteristics of this series and the circuit current characteristics in switching situation of P-side IGBT are described as below.

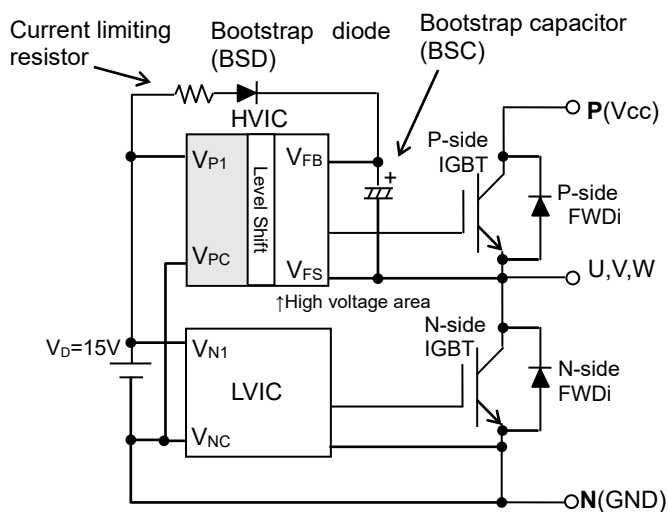


Fig.4-1 Bootstrap Circuit Diagram

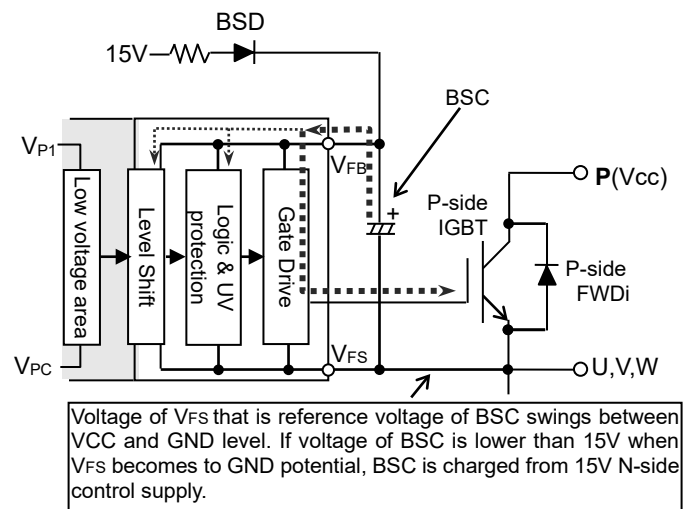


Fig.4-2 Bootstrap Circuit Diagram

4.2 Bootstrap Supply Circuit Current at Switching State

Bootstrap supply circuit current I_{DB} at steady state is maximum 0.55mA for this series. But at switching state, because gate charge and discharge are repeated by switching, the circuit current will exceed 0.55mA and increases proportional to carrier frequency. For reference, Fig.4-3 and Fig.4-4 show the circuit current I_{DB} for P-side IGBT driving supply - carrier frequency f_c typical characteristics for each products.

Conditions: $V_D=V_{DB}=15V$, $T_J=150^{\circ}C$, $V_{CC}=450V$

 


Fig.4-3 I_{DB} vs. Carrier frequency for PSS50SA2F6

 


Fig.4-4 I_{DB} vs. Carrier frequency for PSS75SA2F6

4.3 Note for designing the bootstrap circuit

When each device for bootstrap circuit is designed, it is necessary to consider various conditions such as temperature characteristics, change by lifetime, variation and so on. Note for designing these devices are listed as below. For more detail information about driving by the bootstrap circuit, refer the DIIPM application note "*Bootstrap Circuit Design Manual*"

(1) Bootstrap capacitor

Electrolytic capacitors are used for BSC generally. And recently ceramic capacitors with large capacitance are also applied. But DC bias characteristic of the ceramic capacitor when applying DC voltage is considerably different from that of electrolytic capacitor. (Especially large capacitance type) Some differences of capacitance characteristics between electrolytic and ceramic capacitors are listed in Table 4-1.

Table 4-1 Differences of capacitance characteristics between electrolytic and ceramic capacitors

	Electrolytic capacitor	Ceramic capacitor (large capacitance type)
Temperature characteristics (Ta:-20~ 85°C)	<ul style="list-style-type: none"> Aluminum type: Low temp.: -10% High temp: +10% Conductive polymer aluminum solid type: Low temp.: -5% High temp: +10% 	Different due to temp. characteristics rank Low temp.: -5%~0% High temp.: -5%~-10% (in the case of B,X5R,X7R ranks)
DC bias characteristics (Applying DC15V)	Nothing within rating voltage	Different due to temp. characteristics, rating voltage, package size and so on -70%~-15%

DC bias characteristic of electrolytic capacitor is not matter. But it is necessary to note ripple capability by repetitive charge and discharge, life time which is greatly affected by ambient temperature and so on. Above characteristics are just example data which are obtained from the WEB, please refer to the capacitor manufacturers about detailed characteristics.

(2) Bootstrap diode

This series integrate bootstrap diodes for P-side driving supply. This BSD incorporates current limiting resistor (typ. 20Ω). The V_F - I_F characteristics (including voltage drop by built-in current limiting resistor) is shown in Fig.4-5 and Table 4-2.

 


Fig.4-5 V_F - I_F curve for bootstrap Diode (The right figure is enlarged view)

Table 4-2 Electric characteristics of built-in bootstrap diode

Item	Symbol	Condition	Min.	Typ.	Max.	Unit
Bootstrap Di forward voltage	V_F	$I_F=10\text{mA}$ including voltage drop by limiting resistor	0.5	0.9	1.3	V
Built-in limiting resistance	R	Included in bootstrap Di	16	20	24	Ω

4.4 Initial charging in bootstrap circuit

In the case of applying bootstrap circuit, it is necessary to charge to the BSC initially because voltage of BSC is 0V at initial state or it may go down to the trip level of under voltage protection after long suspending period (even 1s). BSC charging is performed by turning on all N-side IGBT normally. When outer load (e.g. motor) is connected to the DIIPM, BSC charging may be performed by turning on only one phase N-side IGBT since potential of all output terminals will go down to GND level through the wiring in the motor. But its charging efficiency might become lower due to some cause. (e.g. wiring resistance of motor)

There are mainly two procedures for BSC charging. One is performed by one long pulse, and another is conducted by multiple short pulses. Multi pulse method is used when there are some restriction like control supply capability and so on.

 
 



Fig.4-7 Example of waveform by one charging pulse

Initial charging needs to be performed until voltage of BSC exceeds recommended minimum supply voltage 13V. (It is recommended to charge as high as possible with consideration for voltage drop between the end of charging and start of inverter operation.)

After BSC was charged, it is recommended to input one ON pulse to the P-side input for reset of internal IC state before starting system. Input pulse width is needed to be longer than allowable minimum input pulse width $PWIN(on)$. (e.g. 1.5 μ s)

CHAPTER 5 PACKAGE HANDLING


5.1 Packaging Specification

 

Spacers are inserted into the top and bottom of the box.
If there is some space on top of the box, additional buffer materials are also inserted.

Fig.5-1 Packaging Specification

5.2 Handling Precautions

 <h1>Cautions</h1>	
Transportation	<ul style="list-style-type: none"> •Put package boxes in the correct direction. Putting them upside down, leaning them or giving them uneven stress might cause electrode terminals to be deformed or resin case to be damaged. •Throwing or dropping the packaging boxes might cause the devices to be damaged. •Wetting the packaging boxes might cause the breakdown of devices when operating. Pay attention not to wet them when transporting on a rainy or a snowy day.
Storage	<ul style="list-style-type: none"> •We recommend temperature and humidity in the ranges 5-35°C and 45-75%, respectively, for the storage of modules. The quality or reliability of the modules might decline if the storage conditions are much different from the above.
Long storage	<ul style="list-style-type: none"> •When storing modules for a long time (more than one year), keep them dry. Also, when using them after long storage, make sure that there is no visible flaw, stain or rust, etc. on their exterior.
Surroundings	<ul style="list-style-type: none"> •Keep modules away from places where water(including dew condensation) or organic solvent may attach to them directly or where corrosive gas, explosive gas, fine dust or salt, etc. may exist. They might cause serious problems.
Flame resistance	<ul style="list-style-type: none"> •The epoxy resin of case material is flame-resistant type (UL standard 94V-0), but they are not noninflammable.
Anti-electrostatic Measures	<ul style="list-style-type: none"> •ICs and power chips with MOS gate structure are used for the DIIPM power modules. Please keep the following notices to prevent modules from being damaged by static electricity. <p>(1) Precautions against the device destruction caused by the ESD When the ESD of human bodies, packaging and etc. are applied to terminal, it may damage and destroy devices. The basis of anti-electrostatic is to inhibit generating static electricity possibly and quick dissipation of the charged electricity.</p> <ul style="list-style-type: none"> *Containers that charge static electricity easily should not be used for transit and for storage. *Terminals should be always shorted with a carbon cloth or the like until just before using the module. Never touch terminals with bare hands. *Should not be taking out DIIPM from tubes until just before using DIIPM and never touch terminals with bare hands. *During assembly and after taking out DIIPM from tubes, always earth the equipment and your body. It is recommended to cover the work bench and its surrounding floor with earthed conductive mats. *When the terminals are open on the printed circuit board with mounted modules, the modules might be damaged by static electricity on the printed circuit board. *If using a soldering iron, earth its tip. <p>(2) Notice when the control terminals are open</p> <ul style="list-style-type: none"> *When the control terminals are open, do not apply voltage between the collector and emitter. It might cause malfunction. *Short the terminals before taking a module off.
Anti-overvoltage Measures	<ul style="list-style-type: none"> •Precautions for overvoltage destruction. <p>It should be noted that overvoltage destruction of DIIPM might be caused by applying surges to inner chips (power chips and ICs) when surges are impressed to DIIPM package directly or indirectly via the circuit board by surge discharging due to mis-operation on the in-circuit inspection process (e.g. plug off the connector of test board before discharging its capacitor, imperfect contact of the connector, and so on).</p>

Important Notice

The information contained in this datasheet shall in no event be regarded as a guarantee of conditions or characteristics. This product has to be used within its specified maximum ratings, and is subject to customer's compliance with any applicable legal requirement, norms and standards.

Except as otherwise explicitly approved by Mitsubishi Electric Corporation in a written document signed by authorized representatives of Mitsubishi Electric Corporation, our products may not be used in any applications where a failure of the product or any consequences of the use thereof can reasonably be expected to result in personal injury.

In usage of power semiconductor, there is always the possibility that trouble may occur with them by the reliability lifetime such as Power Cycle, Thermal Cycle or others, or when used under special circumstances (e.g. condensation, high humidity, dusty, salty, highlands, environment with lots of organic matter / corrosive gas / explosive gas, or situations which terminals of semiconductor products receive strong mechanical stress). Therefore, please pay sufficient attention to such circumstances. Further, depending on the technical requirements, our semiconductor products may contain environmental regulation substances, etc. If there is necessity of detailed confirmation, please contact our nearest sales branch or distributor.

The contents or data contained in this datasheet are exclusively intended for technically trained staff. Customer's technical departments should take responsibility to evaluate the suitability of Mitsubishi Electric Corporation product for the intended application and the completeness of the product data with respect to such application. In the customer's research and development, please evaluate it not only with a single semiconductor product but also in the entire system, and judge whether it's applicable. As required, pay close attention to the safety design by installing appropriate fuse or circuit breaker between a power supply and semiconductor products to prevent secondary damage. Please also pay attention to the application note and the related technical information.

Keep safety first in your circuit designs!

Mitsubishi Electric Corporation puts the maximum effort into making semiconductor products better and more reliable, but there is always the possibility that trouble may occur with them. Trouble with semiconductors may lead to personal injury, fire or property damage. Remember to give due consideration to safety when making your circuit designs, with appropriate measures such as (i) placement of substitutive, auxiliary circuits, (ii) use of non-flammable material or (iii) prevention against any malfunction or mishap.

Notes regarding these materials

- These materials are intended as a reference to assist our customers in the selection of the Mitsubishi Electric Semiconductor product best suited to the customer's application; they do not convey any license under any intellectual property rights, or any other rights, belonging to Mitsubishi Electric Corporation or a third party.
- Mitsubishi Electric Corporation assumes no responsibility for any damage, or infringement of any third-party's rights, originating in the use of any product data, diagrams, charts, programs, algorithms, or circuit application examples contained in these materials.
- All information contained in these materials, including product data, diagrams, charts, programs and algorithms represents information on products at the time of publication of these materials, and are subject to change by Mitsubishi Electric Corporation without notice due to product improvements or other reasons. It is therefore recommended that customers contact Mitsubishi Electric Corporation or an authorized Mitsubishi Electric Semiconductor product distributor for the latest product information before purchasing a product listed herein. The information described here may contain technical inaccuracies or typographical errors. Mitsubishi Electric Corporation assumes no responsibility for any damage, liability, or other loss rising from these inaccuracies or errors.
Please also pay attention to information published by Mitsubishi Electric Corporation by various means, including the Mitsubishi Electric Semiconductor home page (<http://www.MitsubishiElectric.com/semiconductors/>).
- When using any or all of the information contained in these materials, including product data, diagrams, charts, programs, and algorithms, please be sure to evaluate all information as a total system before making a final decision on the applicability of the information and products. Mitsubishi Electric Corporation assumes no responsibility for any damage, liability or other loss resulting from the information contained herein.
- Mitsubishi Electric Corporation semiconductors are not designed or manufactured for use in a device or system that is used under circumstances in which human life is potentially at stake. Please contact Mitsubishi Electric Corporation or an authorized Mitsubishi Electric Semiconductor product distributor when considering the use of a product contained herein for any specific purposes, such as apparatus or systems for transportation, vehicular, medical, aerospace, nuclear, or undersea repeater use.
- The prior written approval of Mitsubishi Electric Corporation is necessary to reprint or reproduce in whole or in part these materials.
- If these products or technologies are subject to the Japanese export control restrictions, they must be exported under a license from the Japanese government and cannot be imported into a country other than the approved destination.
Any diversion or re-export contrary to the export control laws and regulations of Japan and/or the country of destination is prohibited.
- Please contact Mitsubishi Electric Corporation or an authorized Mitsubishi Electric Semiconductor product distributor for further details on these materials or the products contained therein.